

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T

$$E = \int \frac{C_L V_{dd}^2}{2} \beta f_{clk} + V_{dd} I_{leak} dt$$

Total Energy Consumption

$\int V_{dd} I_{leak} dt$
Static Energy Consumption

$\int \frac{C_L V_{dd}^2}{2} \beta f_{clk} dt$
Dynamic Energy Consumption

Minimize leakage energy by:

- Reducing voltage
- Reducing V_{dd} to GND paths

Minimize active energy by:

- Reducing voltage
- Switching activity
- Capacitance


$$E = \int \frac{C_L V_{dd}^2}{2} \beta f_{clk} + V_{dd} I_{leak} dt$$

Total Energy Consumption

$\int V_{dd} I_{leak} dt$
Static Energy Consumption

$\int \frac{C_L V_{dd}^2}{2} \beta f_{clk} dt$
Dynamic Energy Consumption

 - Reducing supply voltage below nominal
 - Most popular and most effective low-power strategy
 - Voltage-scaling
 - Reduces active power
 - Reduces leakage power (but not necessarily energy/Op)
 - Reduces speed : need to compensate with architectural changes (e.g., parallel processing)



- Various capacitances are merged into a single load capacitor C_L
 - Intrinsic MOS transistor capacitors (driver)
 - Extrinsic (fanout) MOS transistor capacitances
 - Interconnect capacitance

- Energy consumed during one pair of transitions E_{11} :
 - Cross-over currents
 - Charge pumped onto the capacitive load (dominant):
 - $V_{DD} \rightarrow GND$
 - $GND \rightarrow V_{DD}$
- $E_{11} = (C_L V_{dd}) V_{dd} = C_L V_{dd}^2$
 - Independent of transistor geometry (width/length)
 - Independent of the waveforms
 - Quadratic dependency on voltage
- Energy/transition
 - $E_t = C_L V_{dd}^2 / 2$
- Power consumption = Energy/transition * transition/cycle (α) * frequency (f_{clk})
 - $P = \frac{\alpha}{2} C_L V_{dd}^2 f_{clk}$

Extending our calculations to a collection of nodes

- Average energy dissipated per computation cycle for one circuit node

$$E_{ch k} = \frac{\alpha_k}{2} E_{ch cyc k} = \frac{\alpha_k}{2} C_k U_{dd}^2$$

- Average energy dissipated per computation cycle in a voltage domain of K nodes

$$E_{ch} = \sum_{k=1}^K E_{ch k} = U_{dd}^2 \sum_{k=1}^K \frac{\alpha_k}{2} C_k$$

Node activity (aka switching activity)

- Fact: Not all nodes within a (sub)circuit do change state at the same rate.

Definition:

A node's activity α_k indicates how many times per computation cycle node k switches from one logic state to the opposite one when averaged over many computation cycles.

Examples:

- Ungated clock in single-edge-triggered clocking: $\alpha_k = 2$
- Ungated clock in dual-edge-triggered clocking: $\alpha_k = 1$
- Output of a T-type Flip-Flop if permanently enabled: $\alpha_k = 1$
- Output of a D-type Flip-Flop fed with random data: $\alpha_k = 1/2$

Impact of Glitching

- In a synchronous (single-edge triggered) circuit, the activity factor of each node should never rise above $\alpha_k = 1/2$
- Reality: activity factors up to 6 or more can be observed:
 - Increased activity due to glitches: signals reconverge after having propagated along paths of markedly different depths
- Glitching explains why the isomorphic architecture often dissipates more (dynamic) energy than more sophisticated architectures do.
- Activity caused by glitches is very difficult to predict (depends heavily on timing)
 - Analytical prediction almost impossible

- Node activities are distributed very unevenly in most circuits.

 


Figure: Node activities in a lattice filter.

- Activity increases with the number of preceding logic stages (increased glitching)


- Power consumption is divided into
 - Net switching power
 - Internal power
 - Internal power depends on actual input values
 - Power is consumed even if output does not change
- Library files: internal energy characterization for each cell at given supply voltage
 - Internal energy (cross-current, switching) per change in each input and output (as functions of input slope t_{rf} and output load C)
 - Contribution to capacitance of the connected net (input/output load)

$$C = C_{A0I}^Z + C_{net} + C_{INV}^A$$


What about the activity factor(s)?

- Fixed activity:
 - Assume a constant activity factor for all nodes in the circuit
 - Very rough estimate and highly inaccurate
- Statistical power analysis:
 - Assumes a given toggle activity at the input and propagates the activity throughout the circuit using statistical models of the gates
 - Does not account for correlation between signal values
 - No accounting for glitching activity
- Simulation based:
 - Obtains toggle statistics from gate level simulations
 - Most accurate method
 - Slow

Gate-Level Power Analysis Flow

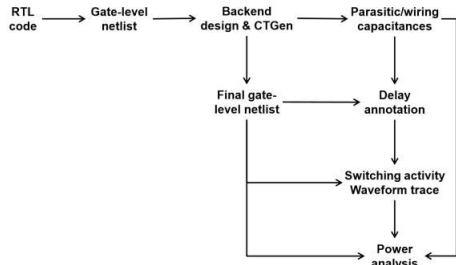


 
- The clock is a major source of power consumption in many synchronous designs



J. Rabaey: Power figures from sever microprocessors and DSPs

RTL Power Reduction: Clocking

 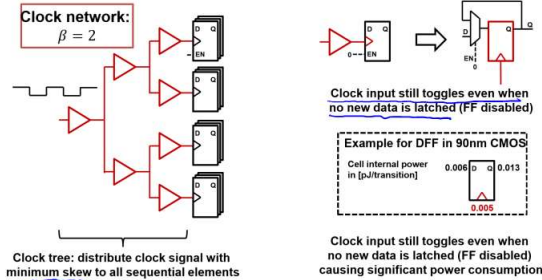
- The clock is a major source of power consumption in many synchronous designs
 - Clock distribution network (clock tree)
 - Intrinsic power of sequential elements (even when data input is constant)



RTL Power Reduction: Clocking




 - Clock gating: reduce power consumption by disabling the clock for
 - Inactive parts of the design (coarse grained)
 - Disabling FFs without consuming internal power (fine-grained)



RTL Power Reduction: Clocking

 - Double-data rate design
 - Clock network has the highest activity factor ($\beta = 2$)
 - Two transitions per clock period with only one transition triggering a state change
- Replace FFs with double-edge triggered FFs
 - Clock frequency can be cut in $\frac{1}{2}$ for same number of operations



- **Silencing: avoid activity in unused logic**
 - Unused logic is not always immediately preceded by registers
 - Avoid changes to the input of unused parts of the logic

Latch-based:

- Silencing immediately effective (no penalty cycle)
- More power while transparent

AND/OR-based:

- Silencing requires one penalty cycle
- Less power while transparent

Leakage Power

- Transistors leak currents even when in off-state

- Sources for leakage
 - Sub-threshold leakage
 - Dominant component in most circuits
 - Gate tunneling
 - Generally low, even in modern technologies due to high-k gate dielectrics
 - Decreases very rapidly with decreasing V_{dd}
 - Junction current
 - Generally low
 - Decreases very rapidly with decreasing V_{dd}

$$P_{total} = \alpha C_{load} V_{DD} \Delta V f_{clock} + V_{DD} (I_{short-circuit} + I_{leakage} + I_{static})$$

↑ DC current drawn from V_{DD} supply

Some statistics

	Intel 80386	DEC alpha21064	cell-based ASIC
Design rule	1.5 μm	0.75 μm	0.5 μm
No of gates	36,808	263,666	10,000
f _{clock}	16 MHz	200 MHz	310 MHz
V_{DD}	5V	3.3V	3V
P_{total}	1.4W	32W	0.8W
Logic gates	32%	14%	9%
clock distrib.	9%	32%	30%
Interconnect	28%	11%	15%
≠/0	26%	37%	43%

$I_{reverse} = A J_s \left(e^{\frac{V_{bias}}{kT/q}} - 1 \right)$

J_s reverse saturation current density
 A junction area

typically $I_{reverse} = 1 \sim 5 \text{ pA}/\mu m^2$
 which increases significantly with temp. T

Leakage Power

- Long channel devices ($>130nm$): $I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$
 - I_{DS} mostly independent from Drain-Source Voltage
 - Leakage current depends strongly on $V_{GS} - V_{th}$
 - Decreasing threshold voltage increases leakage
- Impact of technology scaling on sub-threshold leakage ($<130nm$)
 - Drain-Induced Barrier Lowering (DIBL): V_{DS} modulates threshold voltage
 - I_{DS} becomes a function of V_{DS}

$$V_{GS} - V_{th} + \lambda_{DS} V_{DS}$$
- $I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$

$$I_{leak} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_{DD}}{v_t n}}$$

← Voltage scaling reduces leakage

Leakage Power over Temperature

Drain current depends exponentially on thermal voltage $v_t = kT/q$

$$I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$$

- Exponential I_{DS} increase with temperature

Example: 0.7V, 100nm process, 15mm² die

Vivek De, Intel

Leakage in Transistor Stacks


Stacking occurs

- In many logic gates (> 1 input)
- When introduced intentionally for leakage reduction



$$I_{leak,M1} = I_0 e^{-\frac{-V_M - V_{th} + \lambda_{DS} V_{DD} - V_M}{v_{tH}}}$$

$$I_{leak,M2} = I_0 e^{-\frac{-V_{th} + \lambda_{DS} V_M}{v_{tH}}}$$

Small speed penalty: ~25%

 

Leakage Reduction	
2 NMOS	9 X
3 NMOS	17 X
4 NMOS	24 X
2 PMOS	8 X
3 PMOS	12 X
4 PMOS	16 X

  

Threshold Voltage Selection

- Modern process technologies support devices with different threshold voltages
 - Typically three flavors: low-VT, standard-VT, high-VT
 - Often all three flavors can be mixed in the same design


- VT-selection: tradeoff between speed and leakage

$$t_{pd} = \frac{t_{OX}}{\mu \epsilon_{OX}} \frac{L}{W} C_L \frac{V_{DD}}{(V_{DD} - V_{th})^\alpha}$$

$$I_{leak} = I_0 e^{-\frac{-V_{th} + \lambda_{DS} V_{DS}}{v_{tH}}}$$

- Example: 55nm process

	HVT	SVT	LVT
Delay	20ps	16ps	14ps
Leakage	30nW	60nW	200nW

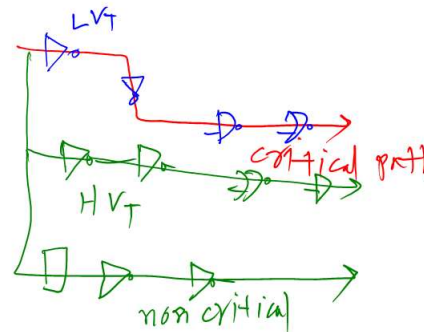


Multi-VT Design

Design tradeoff when choosing a VT flavor:

- Less leakage (high-VT) increases delay and vice versa
- Threshold voltage types can often be mixed

Multi-VT design

 

- Use low-VT cells only on critical paths
- High-VT cells are used in all other paths

Caveat: can be very problematic for near-VT or sub-VT design: path delays scale very differently

Methodology:


- Either done by replacing non-critical cells in the backend OR already during synthesis by providing multiple libraries (HVT/SVT and LVT)

Body Bias Modulates Threshold Voltage

- Body of the transistor is often connected to the source (no body bias)

Introducing a body bias modulates threshold voltage

 
- Forward Body Bias (FBB): increases threshold voltage
- Reverse Body Bias (RBB): reduces threshold voltage









$$V_{th} = V_{th0} - \lambda_{BS} V_{BS} \quad (\eta_{MOS})$$

BULK CMOS:

 - Effect of body bias decreases for technologies below 100nm
- FBB is limited to ~300mV to avoid operating junction diodes in forward direction





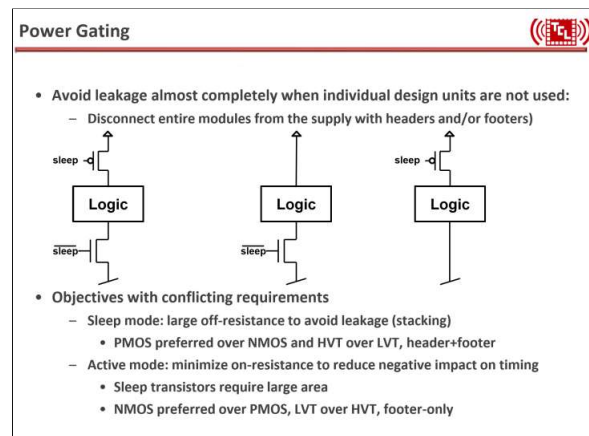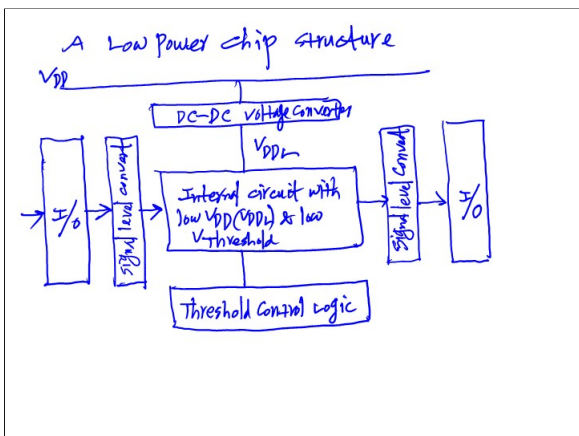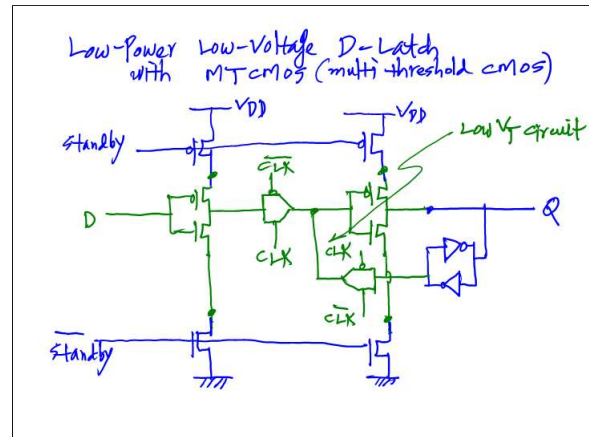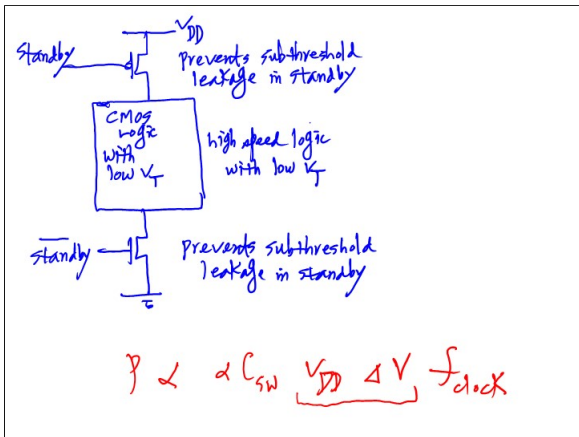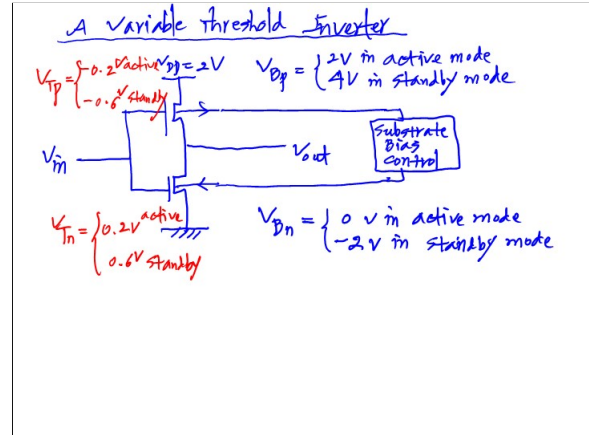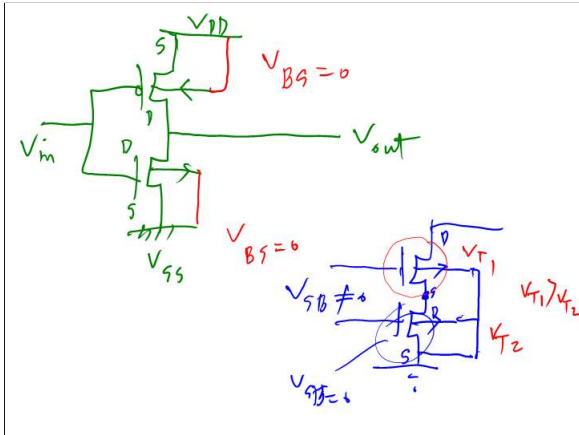

Power Mode Transition



 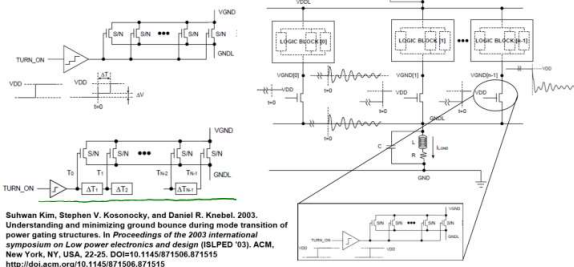- Rapid re-activation of a power gated block can cause large spikes on the supply network of the entire circuit
- Popular solutions:





Ultra-Low-Power Design: Sub-Threshold Operation



- Near/below V_T operation:
 - Exponential delay/leakage increase
 - Minimum energy voltage: balance between leakage and active power consumption

J. Rodrigues, PATMOS 2011, Keynote

  

Given f_{spec} ($\tau < \tau_{spec}$)
 minimize power
 so long as meeting specs

start with high V_T everywhere
 but on timing critical paths,
 lower V_T

Further, you can also adjust V_{DD}
 & play with V_T (bias voltage programming)
 multiple V_{DD} , multiple V_T , etc.