

EE 222 W18 Lecture 13, Feb 27, 2018  
 Controlling  $V_{DD}$  and  $V_{TH}$  for low power

Low power  $\rightarrow$  Low  $V_{DD}$   $\rightarrow$  Low speed  $\rightarrow$  Low  $V_{TH}$   $\rightarrow$  High leakage  $\rightarrow$   $V_{DD}$ - $V_{TH}$  control

	Active	Stand-by
Multiple $V_{TH}$	Dual- $V_{TH}$	MTCMOS
Variable $V_{TH}$	$V_{TH}$ hopping	VTCMOS
Multiple $V_{DD}$	Dual- $V_{DD}$	Boosted gate MOS
Variable $V_{DD}$	$V_{DD}$ hopping	(BPMOS)

Software-hardware cooperation


Technology-circuit cooperation  
 for high  $V_T$ , thicker tox designed for low leakage, boosted gate voltage is applied

- \* MTCMOS: Multi-Threshold CMOS
- \* VTCMOS: Variable Threshold CMOS
- Multiple : spatial assignment
- Variable : temporal assignment


Integrated System Design

21

Dual- $V_{TH}$  concept

 

 Clustered Voltage Scaling (CVS)  
 Conventional Design vs CVS Structure




Once  $V_L$  is applied to a logic gate,  $V_L$  is applied to subsequent logic gates until F/F's to eliminate DC current paths. F/F's restore  $V_H$ .

M. Takahashi et al., "A 60mW MPEG4 Video Codec Using Clustered Voltage Scaling with Variable Supply-Voltage Scheme," ISSCC, pp.36-37, Feb.1998.

$V_{DD}$  should be as low as possible

Energy consumption is proportional to the square of  $V_{DD}$ .

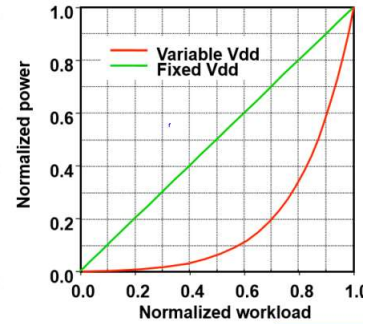$V_{DD}$  should be lowered to the minimum level which ensures the real-time operation.



TransMeta Example

LongRun Technology Demonstration

MHz	Voltage	% Full Power
700	1.65	100%
400	1.4	41%
333	1.2	25%

Power =  $C \times V^2 \times F = 400\text{MHz}/700\text{MHz} \times 1.4V^2/1.65V^2 = 41\%$


- Crusoe processor starts off at 700MHz
- DVD movie requires between 333 and 400MHz
- Power is reduced to 25 or 41% of full power
- The result is extended DVD playtime

TransMeta Example

LongRun Technology in Operation

- Crusoe processor starts off at 700MHz
- Code Morphing software detects user activity
- The software dynamically adjusts MHz and voltage to the most efficient power level

Crusoe Processor AC/DC Modes	
MHz	Voltage
700	1.65
667	1.65
633	1.60
600	1.60
566	1.55
533	1.55
500	1.50
466	1.50
433	1.45
400	1.40
366	1.35
333	1.30
300	1.25
266	1.20
233	1.15
200	1.10

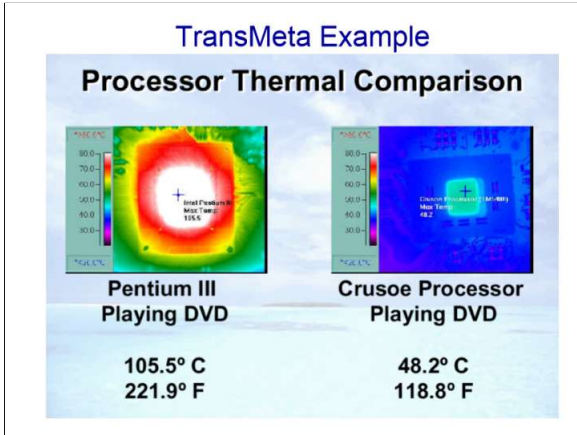

- ### Why is lowering VDD not enough ?
- Total P can be minimized by lower V
    - lower V are a natural result of smaller feature sizes
  - But... transistor speeds decrease dramatically as V is reduced to close to “threshold voltage”
    - performance goals may not be met
    - $t_d = CV / k(V-V_t)^\alpha$  where  $\alpha$  is between 1-2
  - Why not lower this “threshold voltage”?
    - makes noise margin and  $I_{leak}$  worse!
  - Need to do smarter voltage scaling!

- ### Reducing the Supply Voltage: Architectural Approach
- Operate at reduced voltage at lower speed
  - Use architecture optimization to compensate for slower operation
    - e.g. concurrency, pipelining via compiler techniques
  - Architecture bottlenecks limit voltage reduction
    - degradation of speed-up
    - interconnect overheads
  - Similar idea for memory: slower and parallel
- Trade-off AREA for lower POWER**
- C increases but  $V_{DD}$  lowers power.*

### Parallel Datapath

Area = 1476 x 1219  $\mu^2$

- The clock rate can be reduced by x2 with the same throughput:  $f_{par} = f_{ref}/2 = 20$  MHz
- Total switched capacitance =  $C_{par} = 2.15C_{ref}$
- $V_{par} = V_{ref}/1.7$
- $P_{par} = (2.15C_{ref})(V_{ref}/1.7)^2(f_{ref}/2) = 0.36P_{ref}$

### Pipelined Datapath

Area = 640 x 1081  $\mu^2$




- $f_{pipe} = f_{ref}$
- $C_{pipe} = 1.1C_{ref}$
- $V_{pipe} = V_{ref}/1.7$
- Voltage can be dropped while maintaining the original throughput
- $P_{pipe} = C_{pipe} V_{pipe}^2 f_{pipe} = (1.1C_{ref})(V_{ref}/1.7)^2 f_{ref} = 0.37P_{ref}$

### Datapath Architecture-Power Trade-off Summary

Datapath Architecture	Voltage	Area	Power
Original	5V	1	1
Pipelined	2.9V	1.3	0.37
Parallel	2.9V	3.4	0.34
Pipeline-Parallel	2.0V	3.7	0.18

An Ultra Low Power SoC in 14 nm TriGate CMOS (ISSCC 2018 Intel Corp.) for IOT Applications

 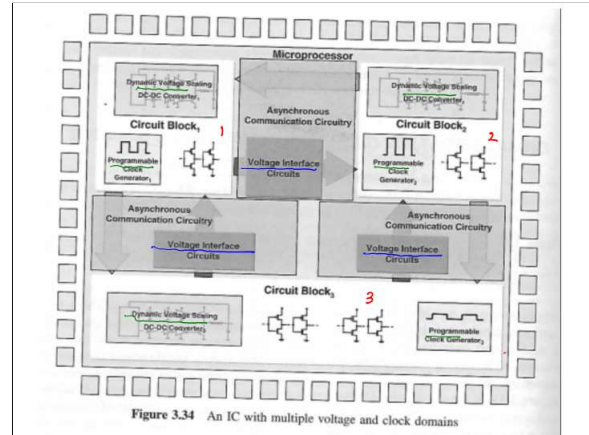 - 2.5 mm x 2.5 mm chip, 12M transistors
- + independent  $V_{DD}$
- 0.55 V for logic, RoM, register-file array
- 0.80 V for dense SRAM array
- 1.05 V for RAM
- 1.70 V for I/O transceivers



As shown in Figure 3.31, for a target clock frequency of 2 GHz, the optimum supply voltage that minimizes the total power consumption of a dual supply and threshold voltage test circuit is 1.2 V. For this supply voltage and for the same clock frequency, the total power consumption of the dual supply and threshold voltage test circuit ( $V_{DD1} = 1.2$  V).



 


Figure 3.29: Power dissipation of dual  $V_{DD}$ /dual  $V_T$  and standard single  $V_{DD}$ /single  $V_T$  test circuits with varying supply voltage for three different clock frequencies, assuming a 100 nm CMOS technology and a 100% activity factor. The supply voltage of the test circuit ( $V_{DD1}$ ) is varied together with the threshold voltage ( $V_{T1}$ ) while maintaining a target clock frequency [5].

A Linear Voltage Regulator

 


 A Switched Capacitor DC-DC Converter (Charge Pump)




1) when  $S_1$  is closed,  $C_1$  charged to  $V_{DD1}$   
 2) when  $S_2$  is closed at  $S_1$  open,  $C_{out}$  is charged to  $2V_{DD1}$ .

A Buck Converter

 
 
$$V_{DD2} = \frac{1}{T_s} \int_0^{T_s} V_C(t) dt$$



$$V_s(s) = L \frac{di}{dt} + v_c \quad (1)$$

$$C \frac{dv_c}{dt} = i \quad (2)$$

$$C \frac{dv_c}{dt} = \frac{di}{dt} \quad (3)$$

$$(3) \rightarrow (1) \quad v_c(s) = LC \frac{d^2 v_c}{dt^2} + v_c$$

$$V_c(s) = LC (s^2 v_c(s) - s v_c(0) - v_c'(0)) + v_c(s)$$



$$V_c(s) = (LC s^2 + 1) v_c(s) - s v_c(0) - v_c'(0)$$

For  $v_c(0) = 0, v_c'(0) = 0, V_s(s) = E U(t) = \frac{E}{s}$  (step input)

$$V_c(s) = \frac{1}{LC s^2 + 1} V_s(s) = \frac{E}{(LC s^2 + 1) s}$$

$$= \frac{(\frac{E}{LC})}{(s^2 + \frac{1}{LC}) s} = \frac{E}{s} + \frac{-E s}{s^2 + \frac{1}{LC}}$$
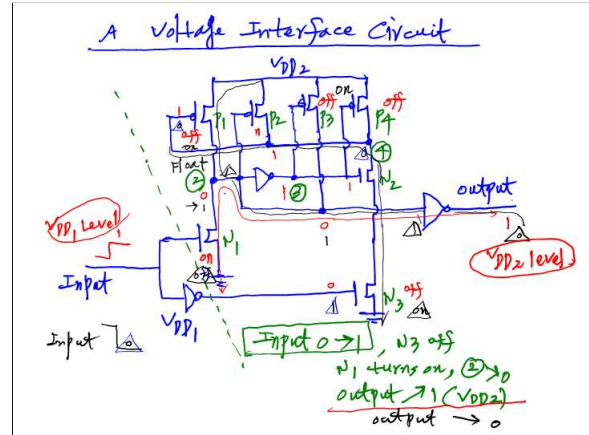 
$$v_c(t) = E [1 - \sin(\frac{1}{\sqrt{LC}} t)]$$



**Combinational Vs. Sequential Circuits**

Combinational (or Combinatorial) Networks/Circuits

- Circuit without storage
- Outputs depend only on its current inputs
- Examples: NAND gate, look-up table (LUT)

Vs.

**Sequential Networks/Circuits**

- Circuit with storage elements
- Outputs depend on present inputs and also on history of inputs
- Examples: RAM, finite state machine (FSM)
- Normally, combinational cells AND storage elements

**Computation in Memory**  
(also called Processing in Memory)

Ref. Convolution-RAM: An Energy Efficient SRAM with Embedded Convolution Computation for Low Power CNN (convolution Neural Network) - based Machine Learning Applications

ISSCC 2018 A. Biswas, et al. MIT

SRAMs for weights storage

Compute RAMs for weight storage + conv. compute

DACs

Registers

Digital comp. unit

Registers



Heavy weight storage


heavy power

less power

less frequent traffic

(conventional)



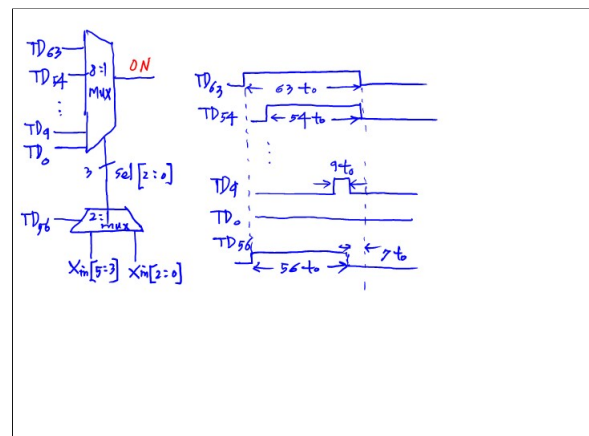
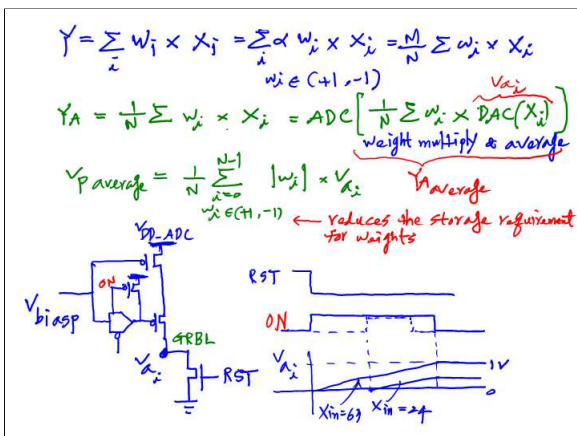


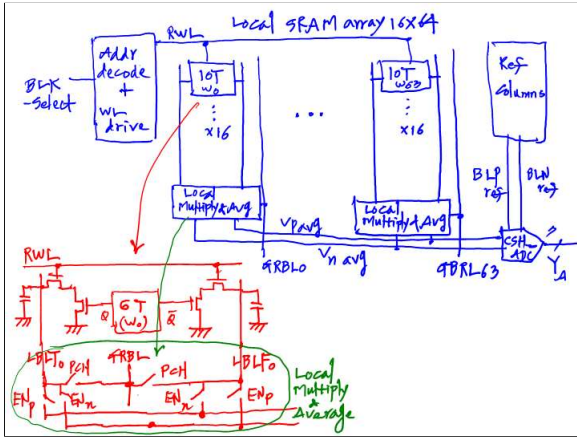

Technology	Machine learning	Comparison mode	Input	Voltage	SRAM size	Thru put
65 nm	CNN	analog	7b	1.2V	2KB	10.7
65 nm	SSCC16	digital	16b	1.2V	26KB	64 TOPS

Energy Efficiency  
28.1 TOPS/Watt  
1.42 TOPS/W


Figure of Merit  
= Throughput x Energy Efficiency  
= 150.3  
2.5

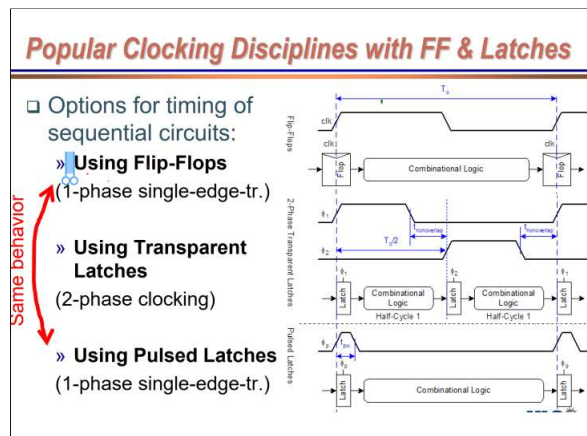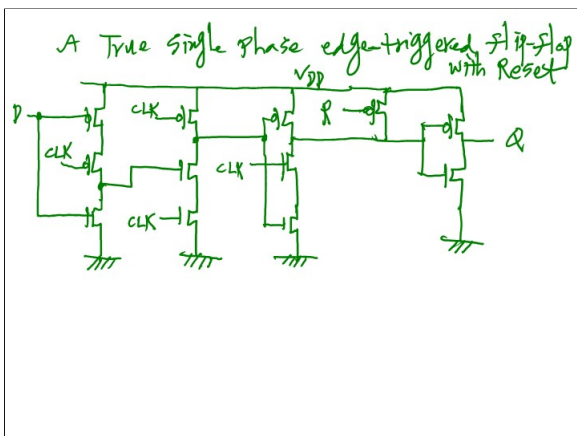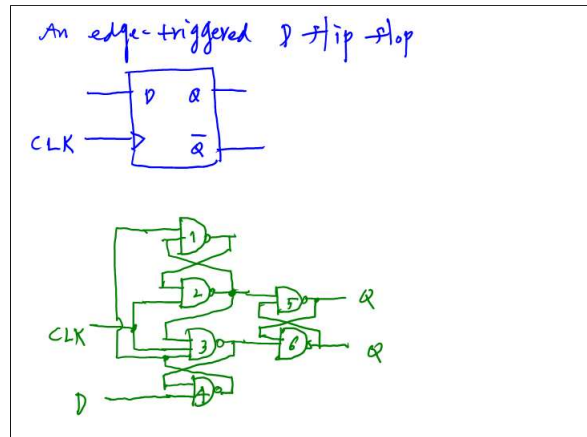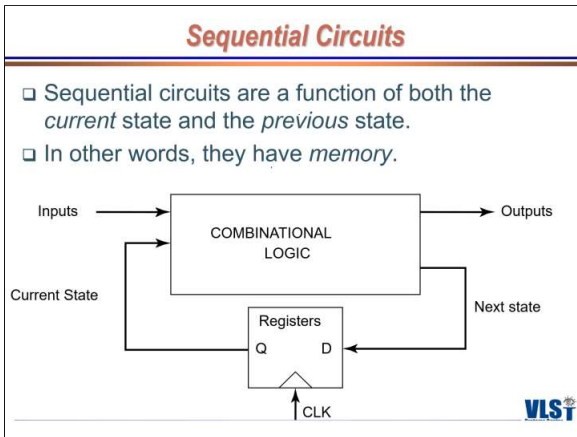
 
## Synchronous Clocking

Definitions:

- ▶ A (sub)circuit is said to operate synchronously iff all state transitions are restricted to occur periodically at precise moments of time that are determined by a special signal referred to as the clock.
- ▶ A clock domain is a (sub)circuit where all clock signals maintain fixed frequency and phase relationships because they are derived from a common source.



## Synchronous Clocking – Design Rules

### Design rule


Consistently dissociate signals into

- ▶ asynchronous reset signals (when to enter the start state)
- ▶ clock signals (when to move from one state to the next)
- ▶ information signals (what state to enter, what output to produce)


### Design rule

Make the clock period long enough so that all transient effects have died out before the next active clock edge instructs registers (and other storage devices) to accept new data!

## Delays - Abstraction

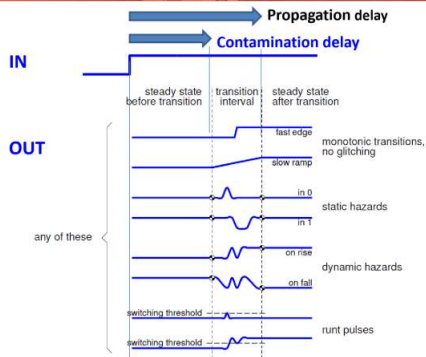
 
## Timing Parameters of Combinational & Sequential Circuits



Combinational circuit with three input signals and three output signals.

$t_{pd}$  (**Propagation delay**): The time required to process new input from applying a stable logic value at a data or clock input until the output has settled on its final value.

$t_{cd}$  (**Contamination delay**): The time from altering the logic value at a data or clock input until the output value starts to change.

## Timing Quantities – Comb. and Seq. Circuits

### Combinational and sequential circuits


#### Propagation delay $t_{pd}$

- New stable input (data or clock) – output settled on final value
- Example NAND: A-to-Z, and B-to-Z
- Example latch: D-to-Q, and/or CLK-to-Q

#### Contamination delay (or retain delay) $t_{cd}$

- Altering input (data or clock) – first change of value at output
- By definition:  $0 \leq t_{cd} \leq t_{pd}$

## Synchronous Timing

 


Synchronous timing:  
All registers synchronized with same CLK

## Timing Constraints (Setup & Hold)


- There are two main problems that can possibly arise in synchronous logic:
  - » **Max Delay:** The data doesn't have enough time to pass from one register to the next before the next clock edge.
  - » **Min Delay:** The data path is so short that it causes a hold violation in capturing register.
- Max delay violations are a result of a slow (long) data paths, including the register's  $t_{su}$ , therefore they are often called "Setup violations".
- Min delay violations are a result of a fast (short) data path, causing the data to change before the  $t_{hold}$  of the reg has passed, therefore they are often called the "Hold violations".
 
## Setup (Max) Constraint

- Let's see what makes up our clock cycle:
  - » After the clock rises, it takes  $t_{cq}$  for the data to propagate to point A.
  - » Then the data goes through the delay of the logic to get to point B.
  - » The data has to arrive at point B  $t_{su}$  before the next clock edge.
- In general, our timing path is a race:
  - » Between the Data Arrival, starting with the launching clock edge.
  - » And the Data Capture, one clock period later.




## Setup (Max) Constraint

 

 
## Hold (Min) Constraint

- Hold problems occur due to the logic changing before  $t_{hold}$  has passed.
- This is not a function of cycle time – it is relative to a single clock edge!
- Example of meeting the hold constraint:
  - » The clock rises and the data at A changes after  $t_{cq}$ .
  - » The data at B changes  $t_{pd}(logic)$  later.
  - » Since the data at B had to stay stable for  $t_{hold}$  after the clock (for the second register), the change at B has to be at least  $t_{hold}$  after the clock edge.




## Hold (Min) Constraint

 


## Summary

- For **Setup** constraints, the clock period has to be longer than the data path delay:
  - » This sets our maximum frequency.  $T > t_{CQ} + t_{logic} + t_{SU}$
  - » If we have setup failures, we can always just **slow down the clock**.
- For **Hold** constraints, the data path delay has to be longer than the hold time:
  - » This is **independent of clock period**.  $t_{CQ} + t_{logic} > t_{hold}$
  - » If there is a hold failure, your chip will never work!
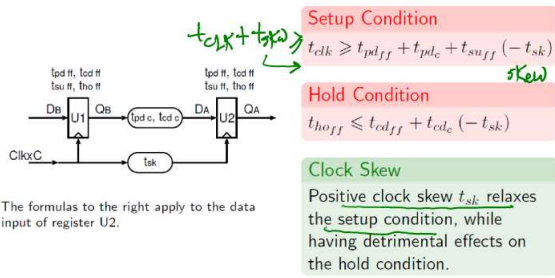
## Fundamental Timing Conditions – Reminder



## Clock Skew and Jitter

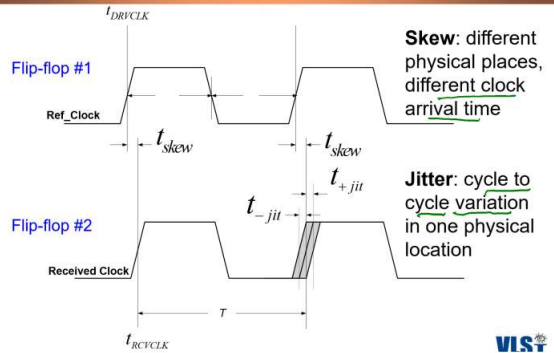

### □ Clock skew

- » Spatial variation in temporally equivalent clock edges; deterministic (can control it) + random,  $t_{sk}$

### □ Clock jitter

- » Temporal variations in consecutive edges of the clock signal; purely random
- » Cycle-to-cycle (short-term)  $t_{js}$
- » Long term  $t_{jl}$


Both skew and jitter affect the effective cycle time

### □ Variation of the pulse width

- » Important for level-sensitive clocking (latches)




## Sources of Clock Uncertainties

 

Sources of clock uncertainty



## Sources of Clock Uncertainties

 


- Disparities of switching thresholds across clocked cells translate ramp times into skew.
- Bistables get characterized for fast clock ramps. Setup and hold times tend to grow when a cell is being clocked with slow ramps.
- Correct behavior and accurate timing are put at risk.

**Avoid slow transitions on clock nets**



 
## Clock Non-Idealities – Waveform Examples



Digital System Clocking: Oklobdzija, Stojanovic, Markovic, Nedovic




## Positive and Negative Skew

 

Positive skew

 Data & clock propagate in the same direction. Relaxed setup constraints (longer effective clock cycle).



Negative skew

Opposite directions. Shorter effective clock cycle.

VLSI

## Setup (Max) Constraint

- The **Launch path** (still) consists of:

$$t_{cq} + t_{logic} + t_{setup}$$

- » But if jitter makes the launch clock later, we need to add it to the data path delay.

$$t_{launch} = t_{CQ} + t_{logic} + t_{SU} + t_{jitter}$$

- The **Capture path** consists of:

- » The clock period ( $T$ )

- » **Positive skew** means the capture clock path is longer.

- » If jitter makes the capture clock earlier, we need to subtract it.

$$t_{capture} = T + \delta - t_{jitter}$$

- Our max constraint is:

$$t_{capture} \geq t_{launch}$$

- So we get:

$$T \geq t_{CQ} + t_{logic} + t_{SU} + 2t_{jitter} - \delta$$

+ $\delta$  Neg. skew


- $\delta$  Pos. skew

Jitter: always worse T

VLSI
 
## Setup (Max) Constraint

- Data has to arrive before *next* active clock edge.



$$T + \delta > t_{CQ} + t_{logic} + t_{SU} + 2t_{jitter}$$

VLSI

## Hold (Min) Constraint

- The **Launch path** (still) consists of:

$$t_{cq} + t_{logic}$$

- » But if jitter makes the launch clock *earlier*, we need to subtract it from the data path delay.

$$t_{launch} = t_{CQ} + t_{logic} - t_{jitter}$$

- The **Capture path** consists of:

- » Skew that makes the clock edge arrive at the capture register later than at the launch register.

- » Actually, since it is a single clock edge, jitter should effect the capture clock the same as the launch clock.

- » But as a worst case, we will add it as spacial jitter.

Clock non-idealities:  
More difficult to meet hold constraint, need longer contamination delay

- Our min constraint is:

$$t_{launch} \geq t_{capture}$$


- So we get:

$$t_{CQ} + t_{logic} \geq \delta + t_{hold} + 2t_{jitter}$$

VLSI
 
## Hold (Min) Constraint


- Data has to arrive *after* same clock edge has arrived at capturing register



$$t_{CQ} + t_{logic} > t_{hold} + \delta + 2t_{jitter}$$


VLSI

## Clock Skew in Alpha Processor

 


- Terrible clock skew
- Zero skew by clock drivers
- Data path in middle has intermediate skew
- Peripherals for I/O has high skew

## EV6 (Alpha 21264) Clocking

 

Global clock waveform (target spec)

 


Next version of Alpha processor had less skew: target >50ps

Insert clock from PLL into center, then H-tree, and more local final clock buffers


Also, implemented more clock gating for power reduction

VLSI

## EV6 Clock Skew

 

## Clock Distribution – H-Tree

 


Equal wire length/number of buffers to get to every location

Clock tree minimizing skew

Clock insertion delay to every FF identical (ideally)

Sometimes: work with “useful (intentional) skew”, e.g. if many FFs have hold violation, to avoid insertion of a large amount of buffers

## More realistic H-tree

 

True H-tree only works for regular structures like FPGAs


But can still have same delay on all paths from source to end points

[Restle98]

## Dealing with Skew and Jitter


- Balance clock paths using regular distribution network, such as H-tree
- Use local clock GRIDS (increased cap and power)
- Route data and clock in opposite directions to improve hold at the expense of setup.
- Shield clock wires (minimize capacitive coupling)
- Use dummy metal density fillers for regular wires
- Use decoupling capacitors (for stable VDD)
- Time borrowing (or cycle stealing): long path borrows time from subsequent short path, accomplished using latches
- “Useful skew” to avoid expensive buffering for hold fix
 
## Additional Timing Parameters of Sequential Circuits


 
### Rising-edge-triggered D-type flip-flop

The value at the input D becomes available at the output Q at the rising edge of the clock



$t_{su}$  (Set-up time): The lapse of time before the active clock edge during which an input is required to assume a fixed logic value of either 0 or 1 at the input of a clocked circuit.

$t_{ho}$  (Hold time): The lapse of time after the active clock edge during which data are required to remain logically unchanged at the input of a clocked circuit.

Data call window:  $t_{su} + t_{ho}$

## Timing Quantities (Cont'd) – Seq. Circuits Only

### Sequential circuits only

#### Setup time $t_{su}$


- Time lapse before active clock edge during which input of bistable element (flip-flop, latch, SRAM, ROM, ...) needs to settle for correct sampling

#### Hold time $t_{ho}$


- Time lapse after active clock edge during which input data of bistable element needs to remain unchanged
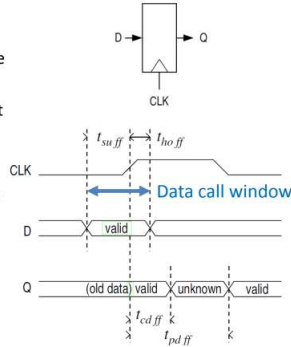
#### Data call window

- Sum of  $t_{su}$  and  $t_{ho}$
- Typically centered around active (positive) clock edge




## A Modern SoC has Many Clock Domains

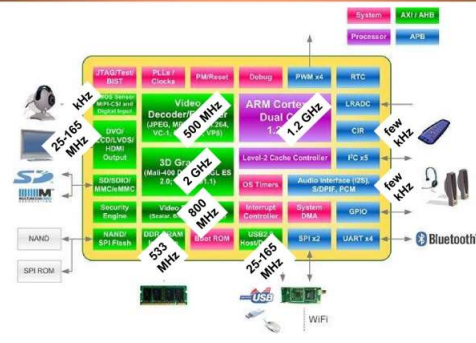

 
## Designs with Multiple Clocks

- Clock domain:** (Sub)circuits in which all clock signals maintain fixed frequency and phase relationship
  - A single clock domain may use multiple divided clocks
- Clock box:** top-level entity that generates all clock signals



 
## Clock Dividers

- Derive a slow clock from a fast clock by dividing it by an integer number (counter)
- Remember: all clocks (including divided clocks) need to be free of hazards and glitches
  - Must assume that any logic can produce glitches
  - Generated (divided) clocks MUST come directly from a FF output



 
## Clock Dividers in the Clock Tree

- Clock and derived clock must be phase aligned at the clock roots
- Clock divider has a delay (FF propagation delay)
  - Need to consider clock divider during clock-tree generation
- Modern clock tree synthesis tools can trace through clock dividers



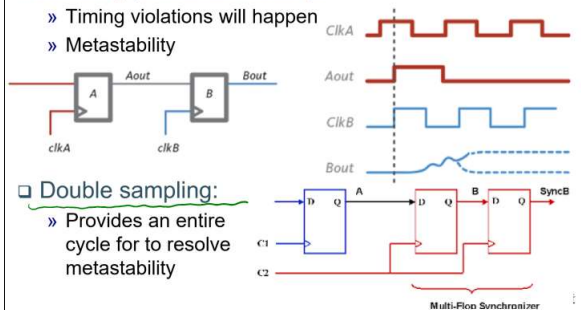
## Crossing Clock Domains

- Arbitrary phase relationship
  - Timing violations will happen
  - Metastability


 
## Clock Gating


- Flip-Flops with ENABLE: prevent FlipFlop(s) from capturing new data
  - » Functional: preserve content over multiple cycles
  - » Power savings: avoid activity in a block that is inactive


 
## Clock Gating

- Advantages:
  - » Saves a multiplexer per FlipFlop with Enable (Area, Delay, and Power advantage)
  - » Avoids activity on the clock net leading to the FlipFlop
  - » Avoids activity on the FlipFlops clock pin reducing internal power consumption
- Disadvantages:
  - » Need for additional logic to suppress the clock while FlipFlop is disabled (area and power penalty)
  - » Need to ensure that the clock signal is free of glitches


- A safe strategy to realize clock gating



- » Latch on the Enable signal shields glitches during the sensitive period of the clock
- » Implemented with individual cells: some timing constraints need to be observed
- » Often realized as single dedicated library cell

 
## Clock Gating

- Coarse grained: disable entire blocks of the design
  - » Inserted manually
- Fine grained: enable for small groups of FlipFlops
  - » Automatic insertion


 
## Improving IO Timing

- Chip provides a clock output that is aligned with the clock at the leaves of the FlipFlops
  - » Output of the clock output pad is declared as clock leaf
  - » Delayed clock is used as a reference for rest of system



## Improving IO Timing

- Delay locked loop (DLL)
  - » Generates a phase shifted clock such that the reference input is phase aligned with the input clock
  - » Clock reference is taken from the leaves of the clock tree
- Internal clock at the leaves is aligned with clock input

