

 
 


EE 222 Lecture 7 Jan 30, 2017


DRAM Memory

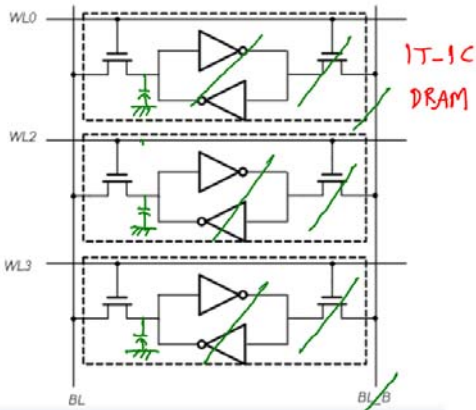


6-transistor SRAM cell

 

 
- Two sides of the bitcell
- Share Horizontal Routing (WWL).
  - Share Vertical Routing (BL, BLB).
  - Share Power and Ground.
  - Word line routed double on Poly and Metal (reduce resistance)



Memory Architecture






 


 Hierarchical Wordline Architecture (DRAM, SRAM)





Slide 7.19  
 The capacitance of a wordline in an SRAM array can be quite large. It consists of the gate capacitance of two access transistors per bit-cell along the row in the array plus the interconnect capacitance of the wires. This capacitance gets even larger if a single wordline is deployed for accessing rows across multiple blocks in a large SRAM macro. To counter this, most large memories use a hierarchical wordline structure similar to the one shown on this slide.

In this structure, the address is divided up into multiple fields to specify the block, block group, and column, for example. The column address is decoded into global wordlines, which are combined with select signals to produce sub-global wordlines. These in turn are gated with the block-select signals to produce the local wordlines. Each local wordline can thus be shorter and have less capacitance. This hierarchical scheme saves power and lowers delay by reducing the amount of capacitance that is switched on the wordline. The approach also allows for additional power savings by preventing wordlines in non-accessed blocks from being activated, which would cause dummy read operations in those blocks.

 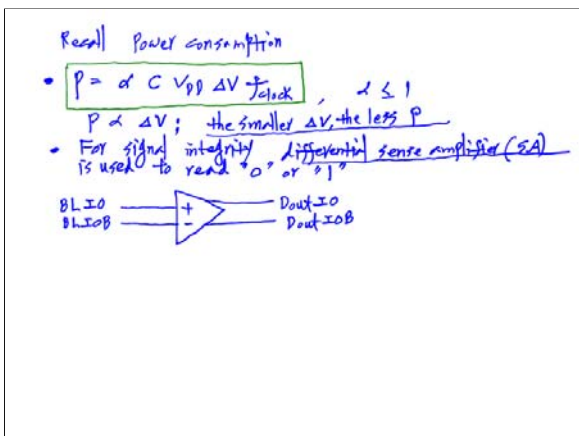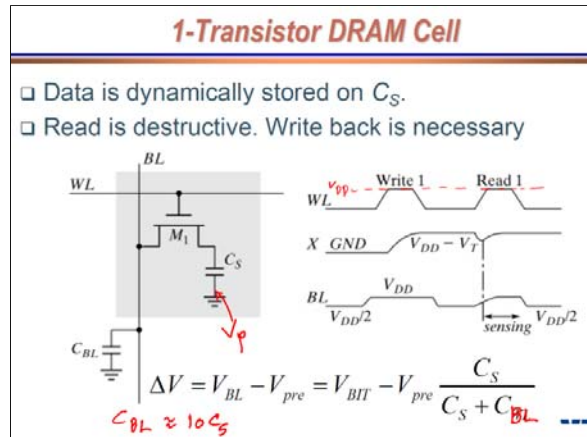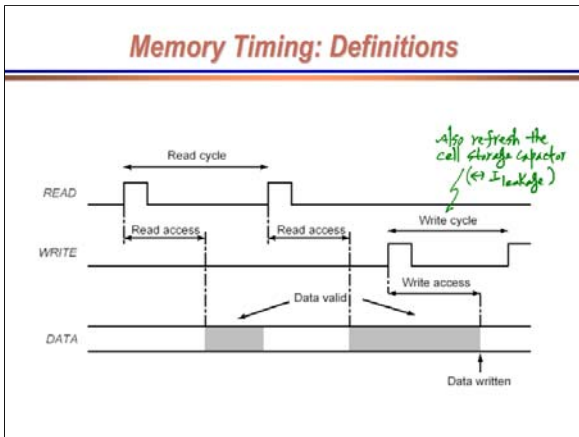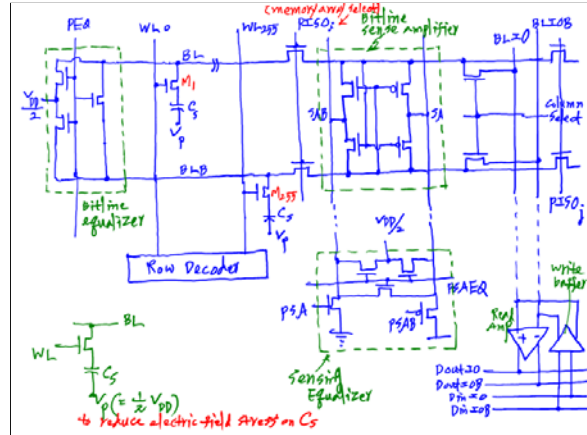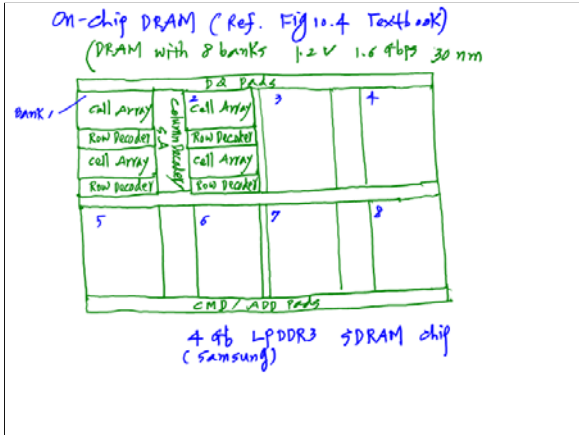


## Advanced 1T1R1C DRAM Cells

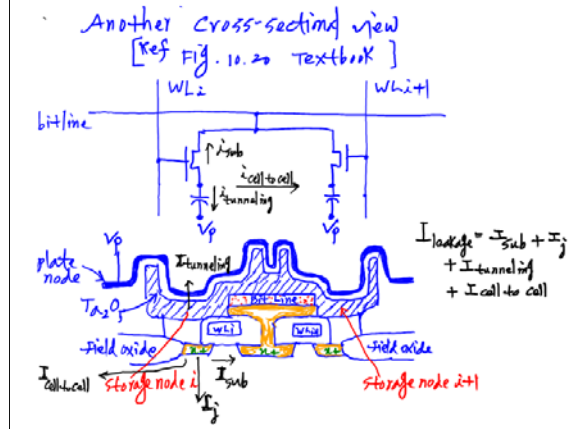 

 
## Clocked Sense Amplifier


- Clocked sense amp saves power
- Requires sense\_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance



## Latch-Based Sense Amplifier (DRAM)


 





 
One side connected to a dummy Bitline with a discharged cell connected as a reference and to increase swing



Initialized in its meta-stable point with EQ. Once adequate voltage gap created, sense amp enabled with SE. Positive feedback quickly forces output to a stable operating point.

## Sense Amp Operation

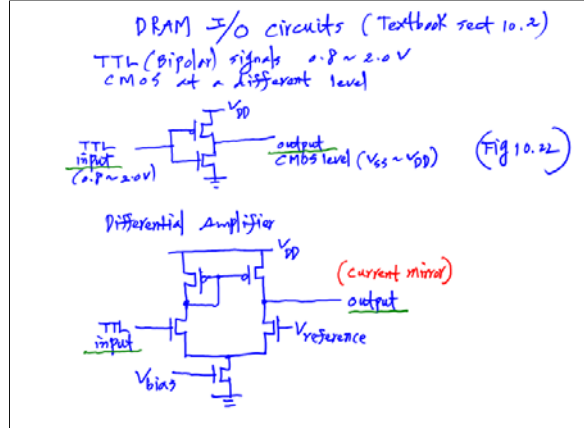 

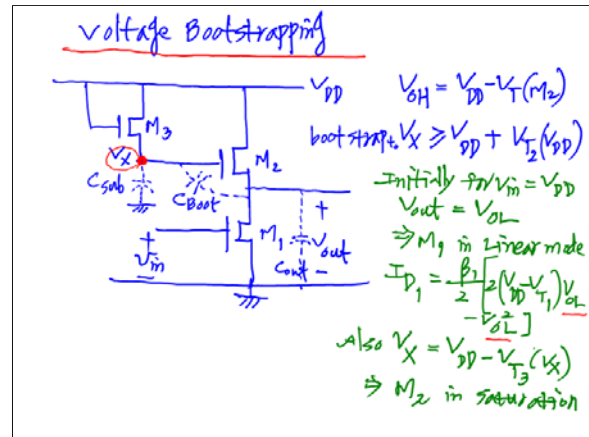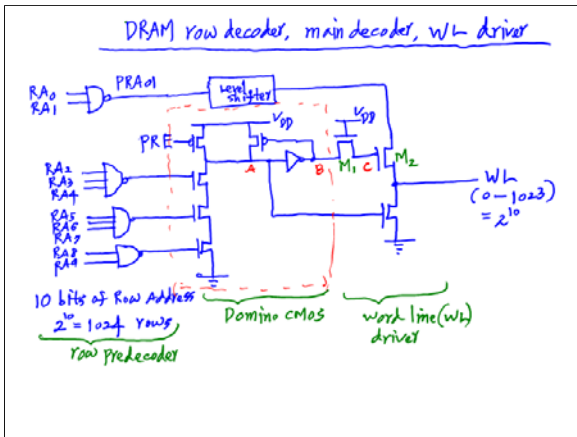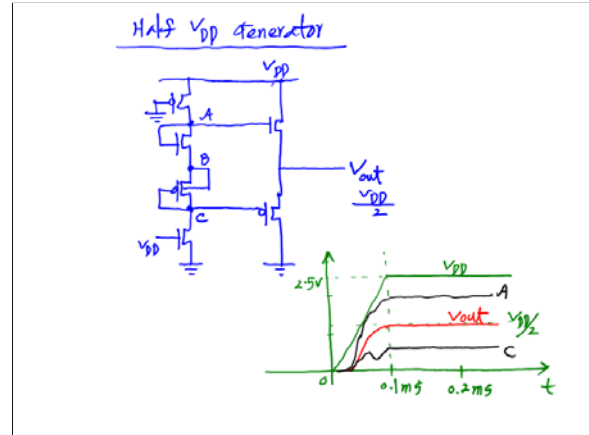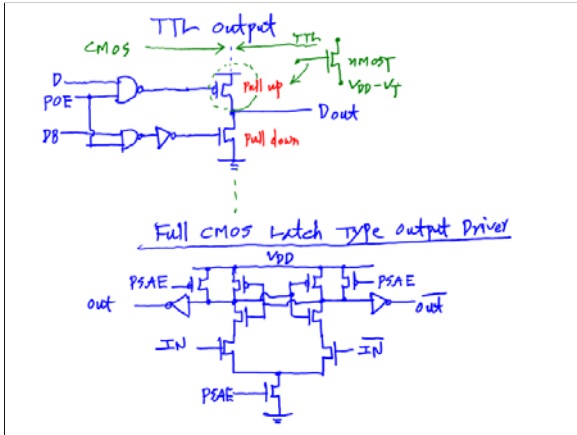

$$I_{D2} = \frac{\beta_2}{2} [V_X - V_{OL} - V_{T2}]^2$$

$$I_{D1} = I_{D2} \Rightarrow V_{OL} \text{ solve for}$$

$$C_{boot} \approx C_{gs}(M_2)$$

Bootstrapping when  $V_{in} = V_{DD} \rightarrow 0$   
 $\Rightarrow V_{out} = V_{OL}$   
 (charged through  $M_2$ )

$\frac{dV_{out}}{dt} > 0$  is coupled to node X  
 to increase  $V_X \Rightarrow V_{out} \rightarrow V_{DD}$

$$\frac{dV_X}{dt} = \frac{C_{boot}}{C_{boot} + C_{sub}} \frac{dV_{out}}{dt}$$

$$\int_{V_{DD} - V_{T3}}^{V_X^{max}} dV_X = \frac{C_{boot}}{C_{boot} + C_{sub}} \int_{V_{OL}}^{V_{DD}} dV_{out}$$


$$V_X^{max} = V_{DD} - V_{OL} + V_{DD} - V_{T3}$$

$$= V_{DD} - V_{T3} + \gamma(V_{DD} - V_{OL})$$

where  $\gamma = \frac{C_{boot}}{C_{boot} + C_{sub}}$

If  $C_{boot} \gg C_{sub}$ , then  $\gamma = 1$

$$V_X^{max} = 2V_{DD} - V_{T3}$$

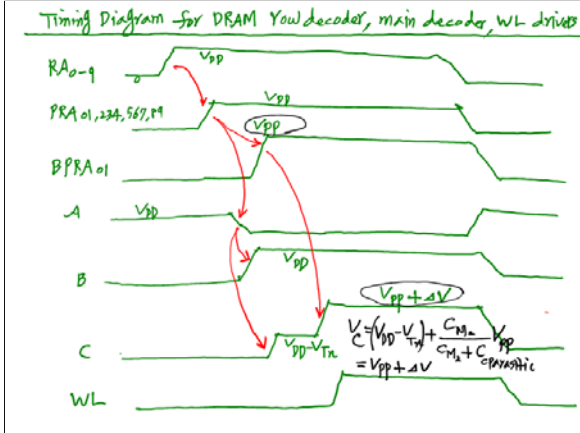

Midterm Exam on Feb. 6

- 1) open book, open computer test
- 2) study HW problems, lecture notes  
calculation of numerical values for C,  $V_T$ , I, etc.
- 3) Derivation of circuit optimization

Proposal due on Feb 6 (in writing)

