 


CMOS Digital Integrated Circuits




Chapter 5 MOS Inverters: Static Characteristics

Y. Leblebici

1


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Ideal Inverter

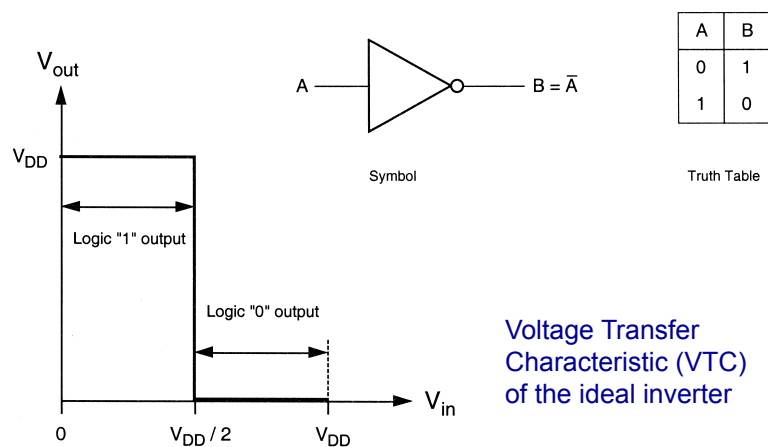


2

Generic Inverter VTC

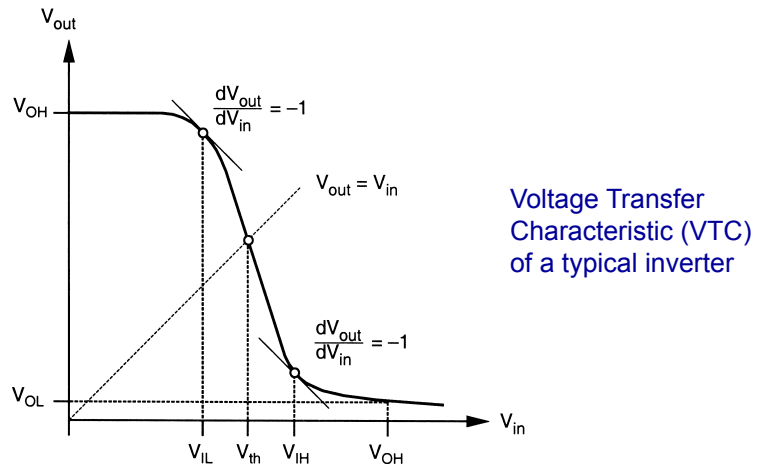

3

Noise Margins

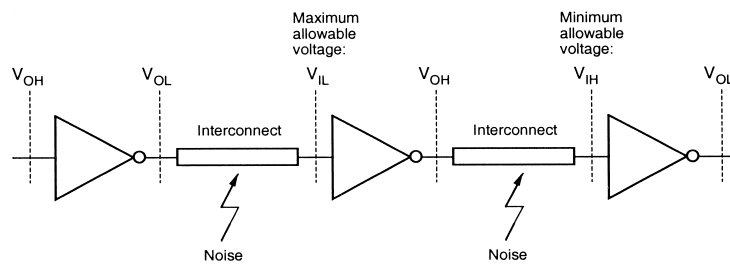


Propagation of digital signals under the influence of noise


- ◆ $V_{OH} : V_{OUT,MAX}$ when the output level is logic "1"
- ◆ $V_{OL} : V_{OUT,MIN}$ when the output level is logic "0"
- ◆ $V_{IL} : V_{IN,MAX}$ which can be *interpreted* as logic "0"
- ◆ $V_{IH} : V_{IN,MIN}$ which can be *interpreted* as logic "1"

4

Noise Margins

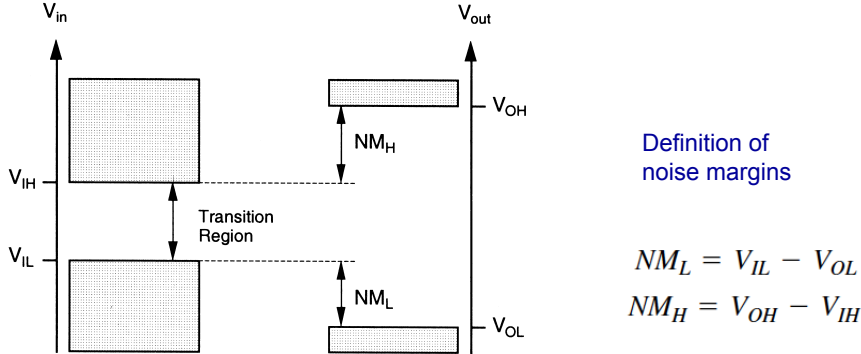

Noise Margins

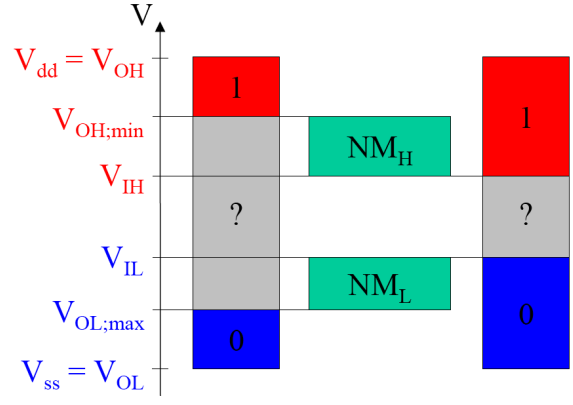

Noise Margins

Nominal output $V_{out} = f(V_{in})$

Output under noise $V'_{out} = f(V_{in} + \Delta V_{noise})$

$$V'_{out} = f(V_{in}) + \frac{dV_{out}}{dV_{in}} \cdot \Delta V_{noise} + \text{higher order terms (neglected)}$$




Perturbed Output = Nominal Output + Gain × External Perturbation

The nominal operating region is defined as the region where the gain is less than unity !


7

CMOS Inverter Circuit

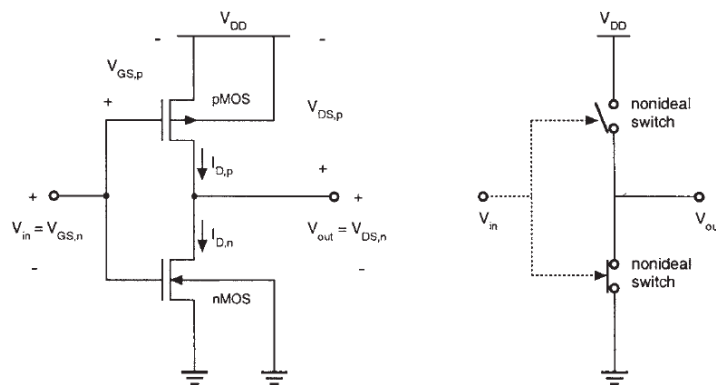

8


CMOS Inverter Circuit

 

The NMOS switch transmits the logic 0 level to the output, while the PMOS switch transmits the logic 1 level to the output, depending on the input signal polarity.


9

CMOS Inverter Circuit

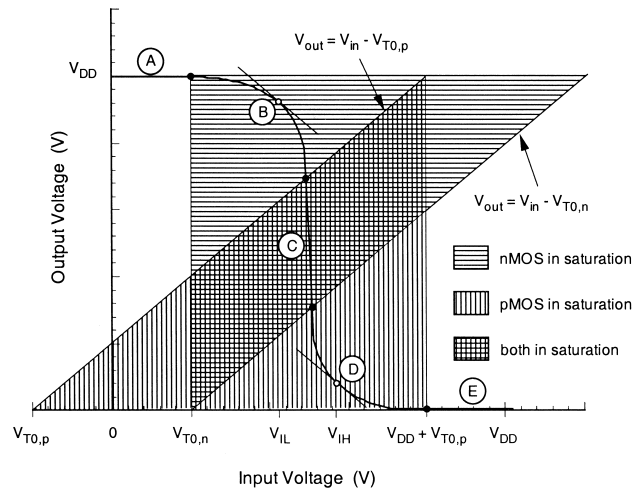

10

CMOS Inverter Circuit

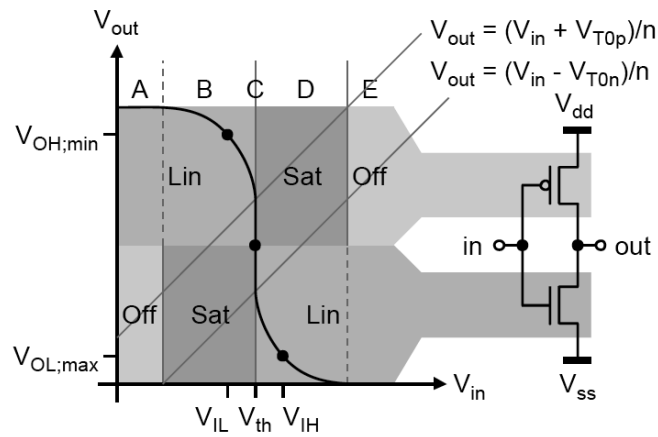

11

CMOS Inverter Circuit

determine noise margins

$$V_{IL} = \frac{2V_{out} + V_{T0,p} - V_{DD} + k_R V_{T0,n}}{1 + k_R} \quad (5.62)$$


$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R \cdot (2V_{out} + V_{T0,n})}{1 + k_R} \quad (5.67)$$

inversion (switching) threshold voltage

$$V_{th} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)} \quad (5.71)$$

12


CMOS Inverter Circuit

 

nMOS transistor current-voltage characteristics

13


CMOS Inverter Circuit

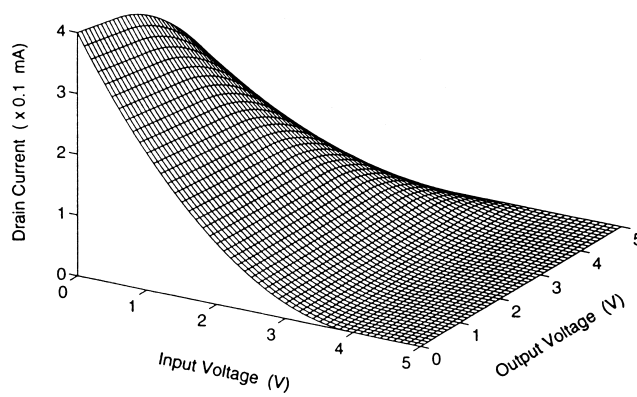

pMOS transistor current-voltage characteristics

14


CMOS Inverter Circuit

 

Intersection of current-voltage surfaces of nMOS and pMOS transistors

15


CMOS Inverter Circuit

 

Intersection of current-voltage surfaces gives the VTC in the voltage plane

16

CMOS Inverter Circuit

 

17

CMOS Inverter Circuit


How to choose the k_R ratio to achieve a desired inversion threshold voltage:

$$k_R = \frac{k_n}{k_p} = \left(\frac{V_{DD} + V_{T0,p} - V_{th}}{V_{th} - V_{T0,n}} \right)^2 \quad (5.73)$$

$$\frac{k_n}{k_p} = \frac{\mu_n C_{ox} \cdot \left(\frac{W}{L} \right)_n}{\mu_p C_{ox} \cdot \left(\frac{W}{L} \right)_p} = \frac{\mu_n \cdot \left(\frac{W}{L} \right)_n}{\mu_p \cdot \left(\frac{W}{L} \right)_p} \quad (5.77)$$


18

CMOS Inverter Circuit

 

19


Supply Voltage Scaling

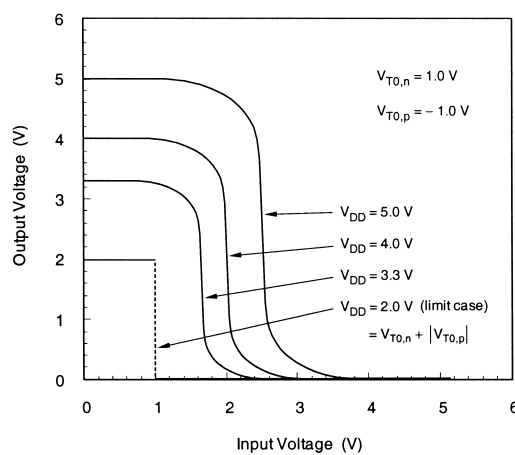



VTC of a CMOS inverter for different power supply voltage values.

20

Dynamic Characteristics of CMOS Inverter

 


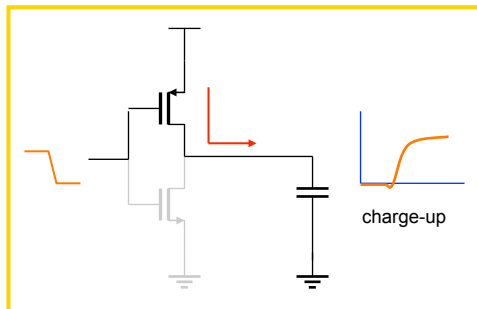 Switching speed determined by the time required to charge-up or charge-down the output load capacitance.



21

Definition of Delay Times

 


The propagation delay times are defined as the time delay between the 50% crossing of the input and the corresponding 50% crossing of the output.

The rise time and the fall time of the output signal are defined as the time required for the voltage to change from its 10% level to its 90% level (or vice versa).


22

Calculation of Propagation Delays

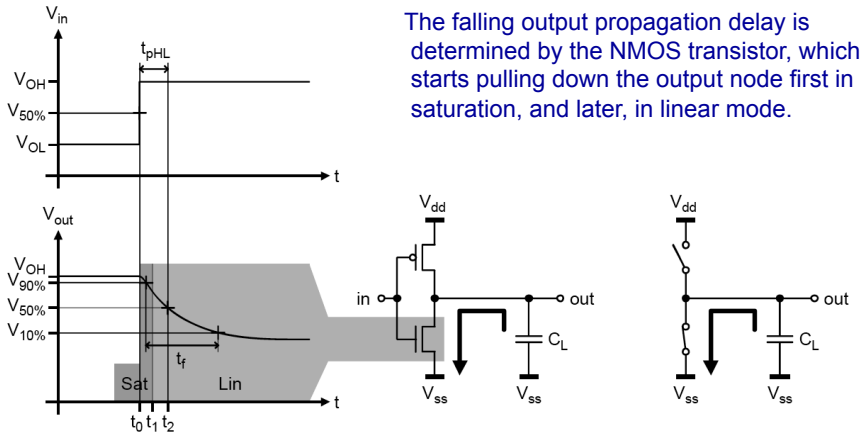


23

Calculation of Propagation Delays

 

24

Calculation of Propagation Delays

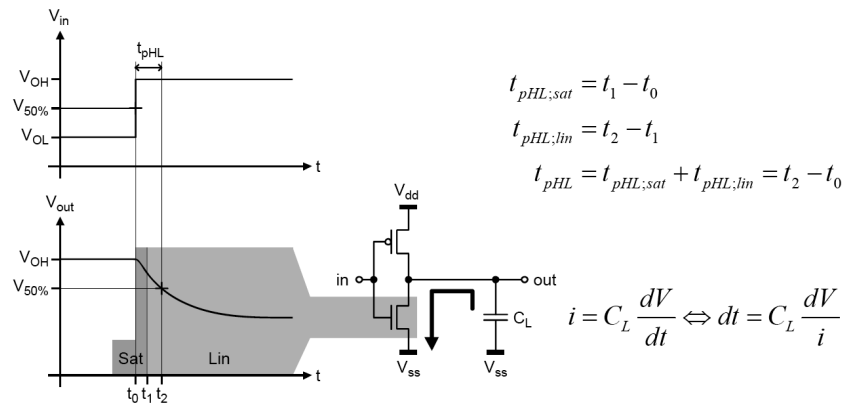

The time required by the NMOS transistor in saturation and in linear region can be calculated separately.

25

Calculation of Propagation Delays


$$t_{pHL:sat} = \frac{2nC_L V_{T0n}}{\beta_n (V_{OH} - V_{T0n})^2}$$

$$t_{pHL:lin} = \frac{nC_L}{\beta_n (V_{OH} - V_{T0n})} \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OL} + V_{OH}} - 1 \right)$$

$$t_{pHL} = t_{pHL:sat} + t_{pHL:lin} = \frac{nC_L}{\beta_n (V_{OH} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OL} + V_{OH}} - 1 \right) \right]$$

26

Calculation of Propagation Delays

 

The time required by the PMOS transistor in saturation and in linear region can be calculated separately.

27

Calculation of Propagation Delays

$$t_{pLH;sat} = \frac{2nC_L V_{T0p}}{\beta_p (V_{dd} - V_{OL} - V_{T0p})^2}$$

$$t_{pLH;lin} = \frac{nC_L}{\beta_p (V_{dd} - V_{OL} - V_{T0p})} \ln \left(\frac{4(V_{dd} - V_{OL} - V_{T0p})}{2V_{dd} - V_{OL} - V_{OH}} - 1 \right)$$

$$t_{pLH} = t_{pLH;sat} + t_{pLH;lin}$$

$$= \frac{nC_L}{\beta_p (V_{dd} - V_{OL} - V_{T0p})} \left[\frac{2V_{T0p}}{V_{dd} - V_{OL} - V_{T0p}} + \ln \left(\frac{4(V_{dd} - V_{OL} - V_{T0p})}{2V_{dd} - V_{OL} - V_{OH}} - 1 \right) \right]$$

28

Calculation of Propagation Delays

$$t_{pHL} = \frac{nC_L}{\beta_n(V_{OH} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{OH} - V_{T0n}} + \ln \left(\frac{4(V_{OH} - V_{T0n})}{V_{OL} + V_{OH}} - 1 \right) \right]$$


$$t_{pLH} = \frac{nC_L}{\beta_p(V_{dd} - V_{OL} - V_{T0p})} \left[\frac{2V_{T0p}}{V_{dd} - V_{OL} - V_{T0p}} + \ln \left(\frac{4(V_{dd} - V_{OL} - V_{T0p})}{2V_{dd} - V_{OL} - V_{OH}} - 1 \right) \right]$$

Summary:

The propagation delay times are proportional to the load capacitance, and inversely proportional to the pull-up (or pull-down) transconductance.

29

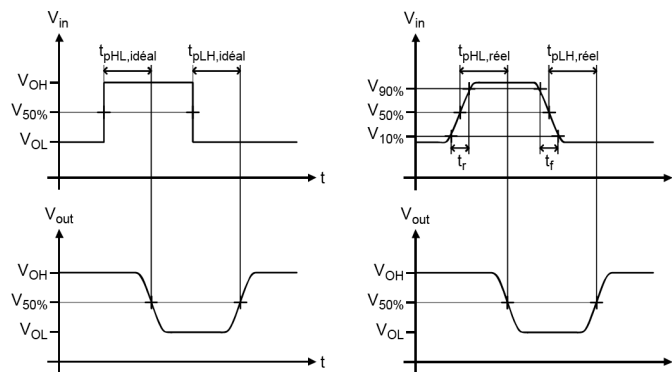
Influence of Nonzero Input Rise/Fall Time



$$t_{pHL, \text{réel}} = \sqrt{t_{pHL, \text{idéal}}^2 + \left(\frac{t_r}{2}\right)^2} \quad t_{pLH, \text{réel}} = \sqrt{t_{pLH, \text{idéal}}^2 + \left(\frac{t_f}{2}\right)^2}$$

30

 Components of the Output Load Capacitance




31

Increasing the Switching Speed

- Need to increase the amount of charge-up and charge-down current that switches the output.
- Increase the transistor (W/L) ratios both in the pull-up path and in the pull-down path.
- However: increasing transistor dimensions will influence the parasitic MOSFET capacitances.
- **The switching speed of a classical CMOS gate is ultimately limited by its intrinsic delay.**

32

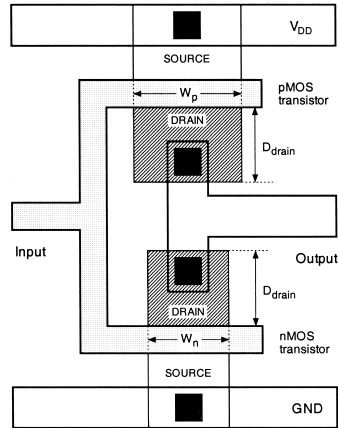

Drain parasitics are mainly responsible for the intrinsic gate delay.

$$\begin{aligned}
 C_{load} &= C_{gd,n}(W_n) + C_{gd,p}(W_p) \\
 &\quad + C_{db,n}(W_n) + C_{db,p}(W_p) \\
 &\quad + C_{int} + C_g \\
 &= f(W_n, W_p)
 \end{aligned}$$

A closer look at the typical CMOS inverter

33

Parasitic Capacitance Components

Drain parasitics:

$$C_{db,n} = W_n D_{drain} C_{j0,n} K_{eq,n} + 2(W_n + D_{drain}) C_{jsw,n} K_{eq,n}$$

$$C_{db,p} = W_p D_{drain} C_{j0,p} K_{eq,p} + 2(W_p + D_{drain}) C_{jsw,p} K_{eq,p}$$

Total capacitive load:

$$\begin{aligned}
 C_{load} &= (W_n C_{j0,n} K_{eq,n} + W_p C_{j0,p} K_{eq,p}) D_{drain} \\
 &\quad + 2(W_n + D_{drain}) C_{jsw,n} K_{eq,n} \\
 &\quad + 2(W_p + D_{drain}) C_{jsw,p} K_{eq,p} \\
 &\quad + C_{int} + C_g
 \end{aligned}$$

34

Parasitic Capacitance Components

$$C_{load} = \alpha_0 + \alpha_n W_n + \alpha_p W_p$$

$$\alpha_0 = 2D_{drain}(C_{jsw,n}K_{eq,n} + C_{jsw,p}K_{eq,p}) + C_{int} + C_g$$

$$\alpha_n = K_{eq,n}(C_{j0,n}D_{drain} + 2C_{jsw,n})$$

$$\alpha_p = K_{eq,p}(C_{j0,p}D_{drain} + 2C_{jsw,p})$$

35

Propagation Delays

$$\left. \begin{array}{l} \text{rising input} \\ \text{falling output} \end{array} \right\} \tau_{PHL} = \left(\frac{\alpha_0 + \alpha_n W_n + \alpha_p W_p}{W_n} \right) \times \left(\frac{L_n}{\mu_n C_{ox}(V_{DD} - V_{T,n})} \right) \times \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$

$$\left. \begin{array}{l} \text{falling input} \\ \text{rising output} \end{array} \right\} \tau_{PLH} = \left(\frac{\alpha_0 + \alpha_n W_n + \alpha_p W_p}{W_p} \right) \times \left(\frac{L_p}{\mu_p C_{ox}(V_{DD} - |V_{T,p}|)} \right) \times \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$

36

Propagation Delays

rising input
falling output

$$\tau_{PHL} = \Gamma_n \left(\frac{\alpha_0 + (\alpha_n + R\alpha_p)W_n}{W_n} \right)$$

falling input
rising output

$$\tau_{PLH} = \Gamma_p \left(\frac{\alpha_0 + \left(\frac{\alpha_n}{R} + \alpha_p \right) W_p}{W_p} \right)$$

Notice that with increasing transistor width W_n and W_p , both delays asymptotically approach fixed limit values, independent of external loads.

37

Propagation Delays

$$\Gamma_n = \left(\frac{L_n}{\mu_n C_{ox} (V_{DD} - V_{T,n})} \right) \times \left[\frac{2V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$

$$\Gamma_p = \left(\frac{L_p}{\mu_p C_{ox} (V_{DD} - |V_{T,p}|)} \right) \times \left[\frac{2|V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$


Intrinsic delay limits will decrease for

- Smaller gate length L
- Larger μ and C_{ox}

But for a given technology, the limits are fixed.


38

 Improving propagation delay times by transistor sizing




39

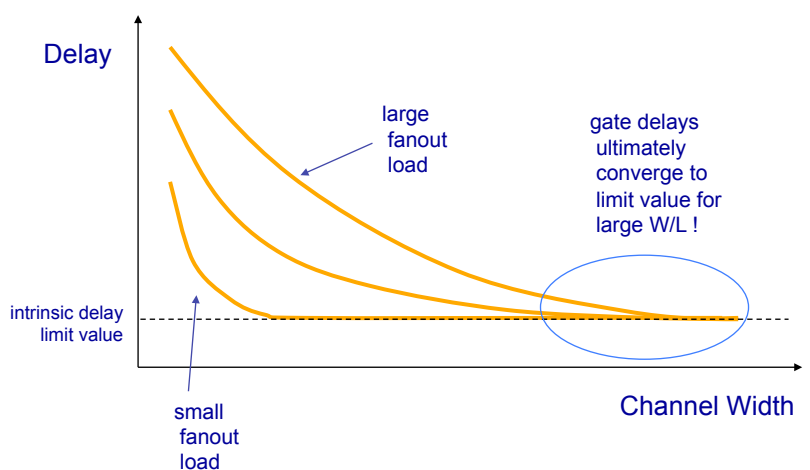Improving propagation delay times by transistor sizing




40

CMOS Inverter Layout

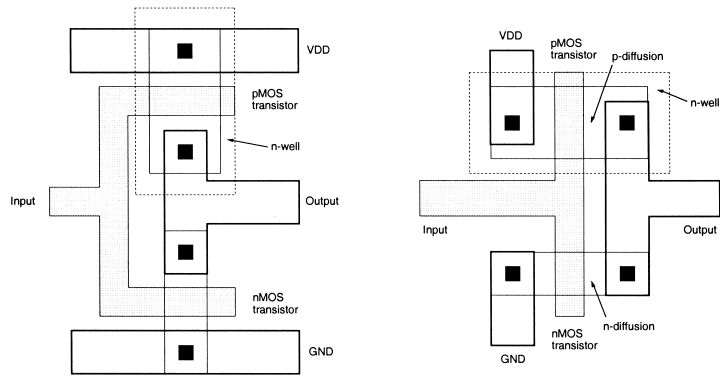

41

CMOS Inverter Layout

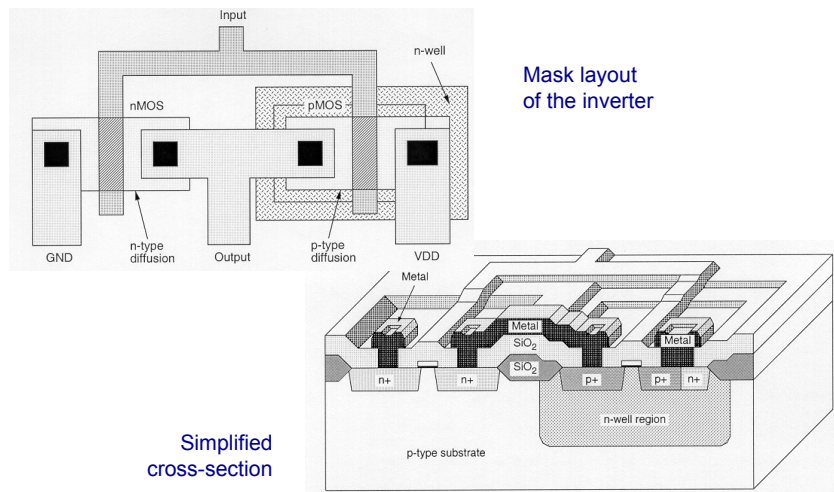

42