
Fundamentals of VLSI

CMOS Power Consumption



Andreas Burg

Telecommunications Circuits Laboratory





ÉCOLE POLYTECHNIQUE
FÉDÉRALE DE LAUSANNE


- **Mobile devices: energy-efficiency**

 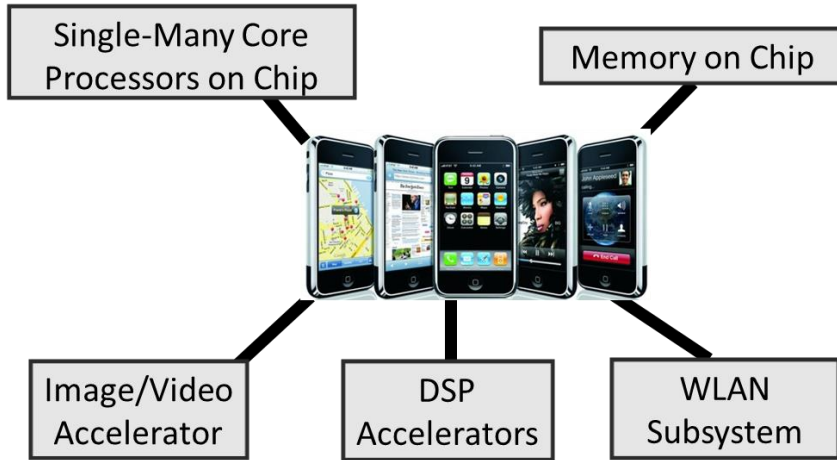

- **Battery capacity grows only very slowly**

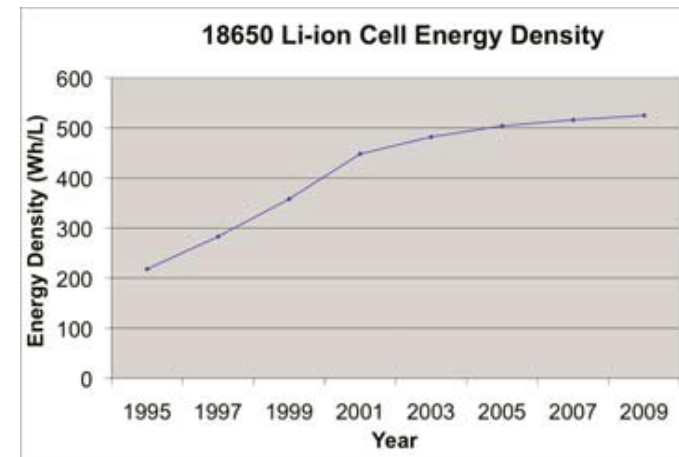 - Boost in the 1990s due to Mobile Phone introduction
- Capacity growth stalled since 2000 at the limit of Li-ion
- Only 3%-7% annual improvement



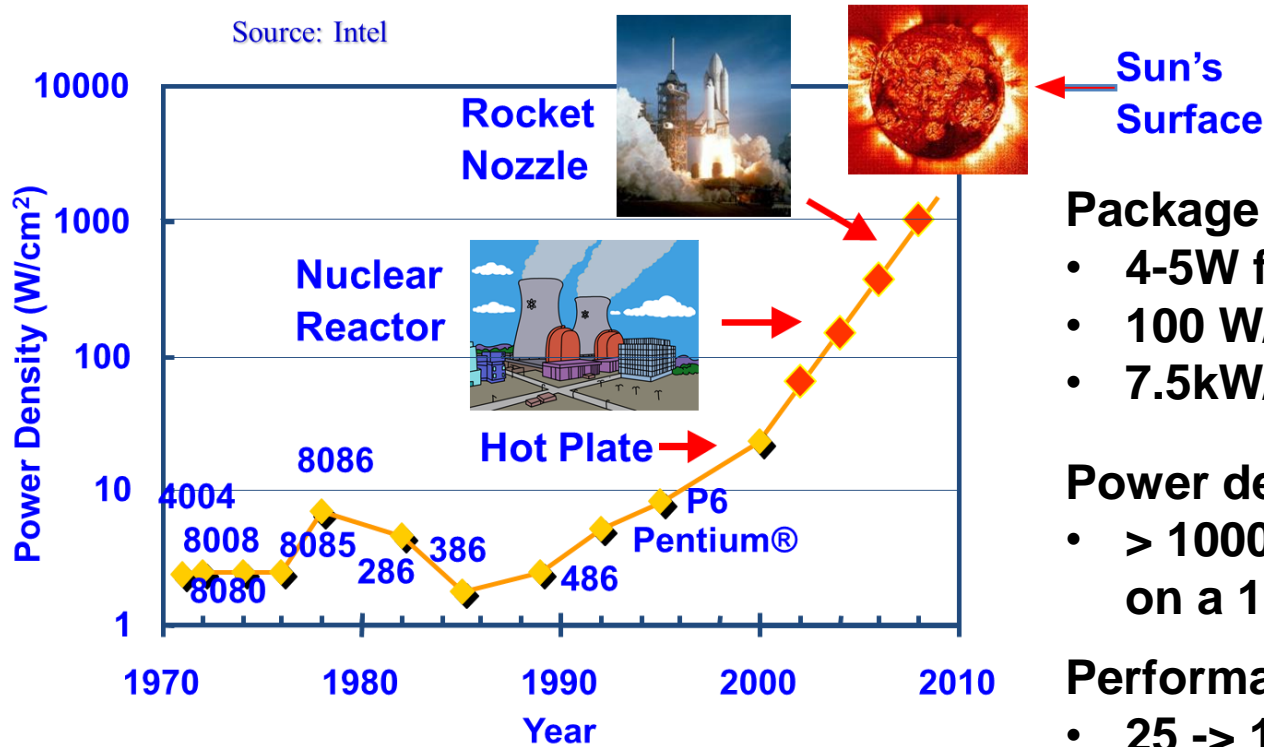

Package cost

- 4-5W for cheap packages
- 100 W/cm² for air cooling
- 7.5kW/rack


Power delivery

- > 1000 pins for power delivery on a 100W processor

Performance penalty

- 25 -> 100 deg. C : 30%

 - **Thermal Design Power:** upper limit on power consumption
 - Microprocessors for servers: ~30-100 W/cm²
 - Mobile devices: ~3W total (handheld)




Complex, large and costly power supply circuits: Three-phase step-down converter built from toroidal coils, power MOSFETs, and electrolytic capacitors.

- **High-performance circuits**

- How to get the heat out?
- How to supply massive currents at very low voltages?
- How to avoid critical voltage drops on supply rails?

- **Battery-operated circuits**

 - How long can we operate a device on a battery charge?



Basics in CMOS Power Consumption and Low Power Design



- **Active Power Consumption in CMOS**
- **Leakage Power Consumption**
- **Voltage Scaling and Sub-VT Design**

- **Four phenomena dissipate energy in digital CMOS circuits**

- Charging and discharging of capacitive loads
 - Crossover currents
 - Leakage currents
 - (Driving of resistive loads)
- } Power
- } Energy

Active Power Consumption in CMOS

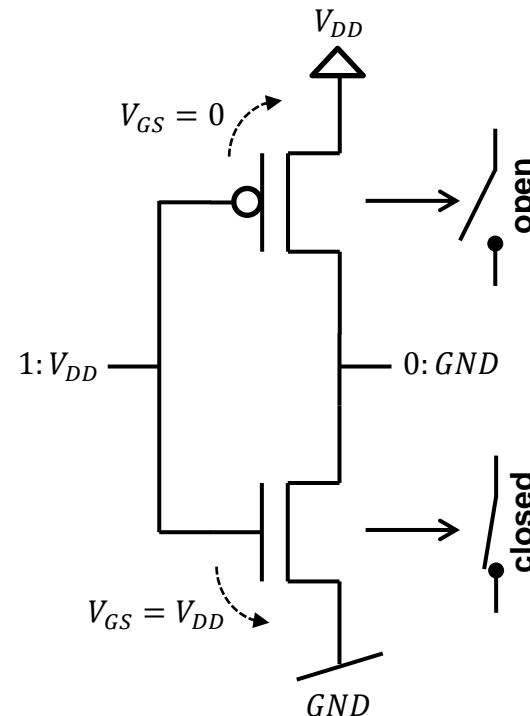 - PMOS performs pull-up to V_{DD}
- NMOS performs pull-down to GND
- **Complementary gate:** output connected to either V_{DD} or GND
 - **Static (steady state)**



- Ideally, no current path from V_{DD} to GND
- Ideally, no static power consumption

The gain factor β is a function of **process parameters** and **layout geomerty**

$$\beta = \frac{\mu \epsilon_{OX}}{t_{OX}} \frac{W}{L}$$

where

t_{OX} gate dielectric thickness
 ϵ_{OX} gate dielectric permittivity
 μ effective carrier mobility in inversion layer

W channel (gate) width
 L channel (gate) length } **Design parameters**


- **Designer sets the drive-strength by controlling width and length of the transistor**

CMOS Inverter: In-Out Transfer Characteristic (Static)




Inverter as non-linear amplifier with a large, but finite gain in the transition region

range	applies when	n-channel ▼	p-channel ▲
A	$0 \leq U_{inp} \leq U_{th n}$	subthreshold	linear
B	$U_{th n} < U_{inp} < U_{inv}$	saturation	linear
C	$U_{inp} \approx U_{inv}$	saturation	saturation
D	$U_{inv} < U_{inp} < U_{dd} + U_{th p}$	linear	saturation
E	$U_{dd} + U_{th p} \leq U_{inp} \leq U_{dd}$	linear	subthreshold

 


Dominant during transition region

 


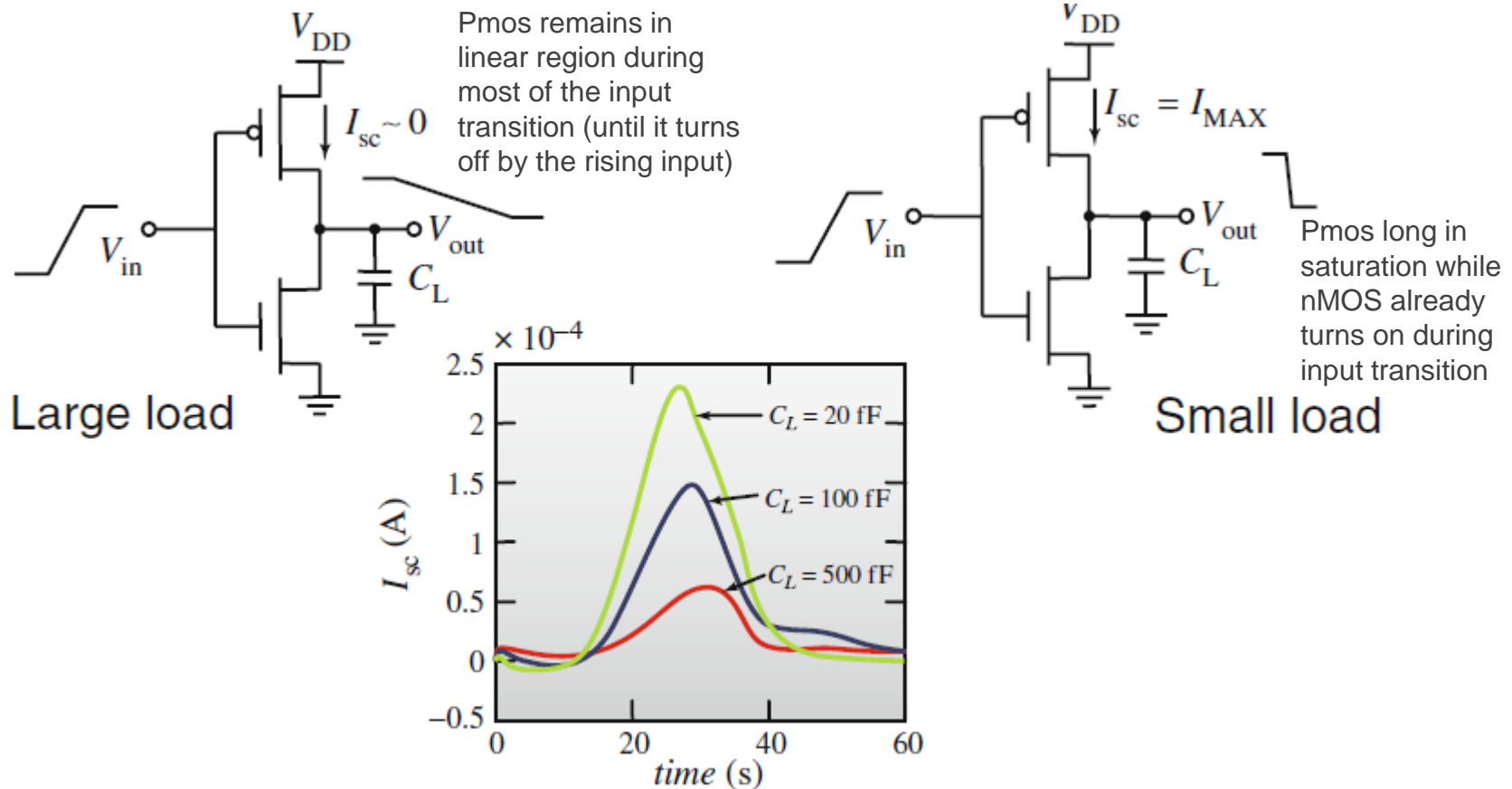(a) Transfer characteristic (b) Crossover current (c) Logic states

- Cross-over currents lead to power consumption during transients



 - Fast input slow output: driving device quickly shuts off completely
- Slow input fast output: driving device remains long in linear region
- Input of one device is output of the other device: balance input-output delay for optimum power consumption



Wider transistors increase the gain factor (drive) but also increase the load (capacitance)

- Various capacitances are merged into a single load capacitor C_L
 - **Intrinsic** MOS transistor capacitors (driver)
 - **Extrinsic (fanout)** MOS transistor capacitances
 - **Interconnect** capacitance

- Energy consumed during one pair of transitions $E_{\downarrow\uparrow}$:

- Cross-over currents
- Charge pumped onto the capacitive load (dominant):

- $E_{\downarrow\uparrow} = (C_L V_{dd}) V_{dd} = C_L V_{dd}^2$


- independent of transistor geometry (width/length)
- Independent of the waveforms
- **quadratic dependency on voltage**

- Energy/transition


- $E_t = C_L V_{dd}^2 / 2$

- Power consumption = Energy/transition * transition/cycle (α) * frequency (f_{clk})

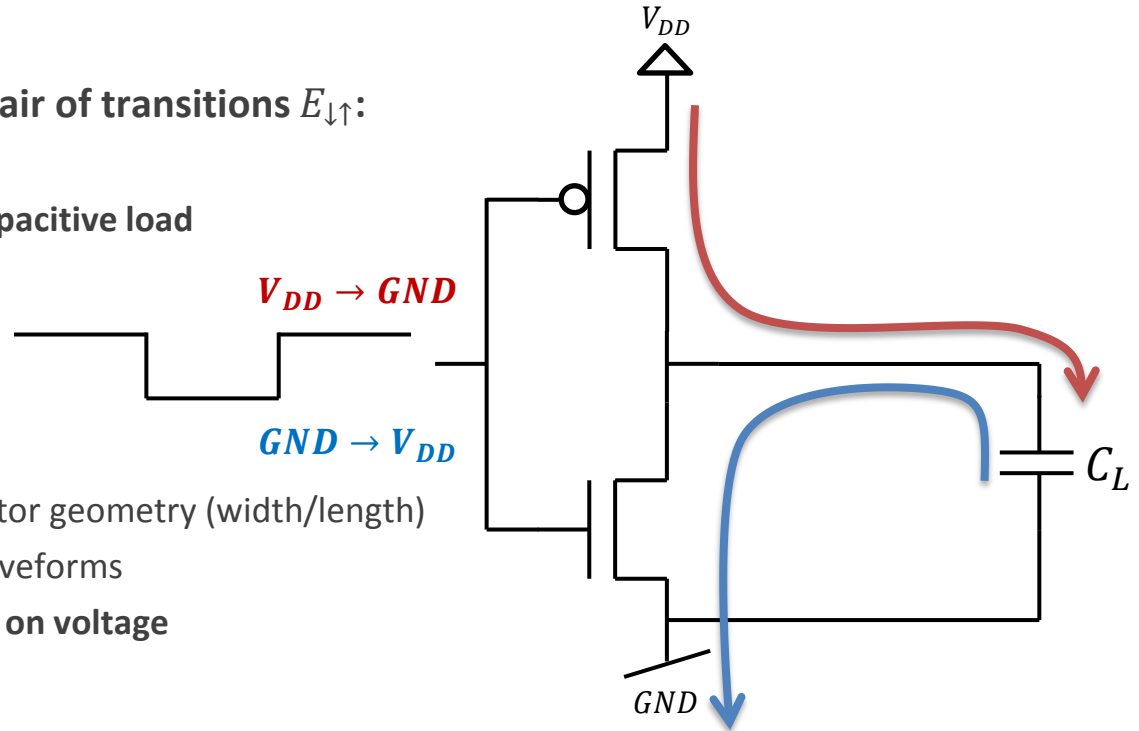- $P = \frac{\alpha}{2} C_L V_{dd}^2 f_{clk}$




- Power consumption is divided into
 - Net switching power
 - Internal power:
 - Internal power depends on actual input values
 - Power is consumed even if output does not change
- Library files: internal energy characterization for each cell at given supply voltage
 - Internal energy (cross-current, switching) per change in each input and output (as functions of input slope t_{rf} and output load C)
 - Contribution to capacitance of the connected net (input/output load)

 

$$C = C_{AOI}^Z + C_{net} + C_{INV}^A$$




What about the activity factor(s)?

- **Fixed activity:**
Assume a constant activity factor for all nodes in the circuit
 - Very rough estimate and highly inaccurate
- **Statistical power analysis:**
Assumes a given toggle activity at the input and propagates the activity throughout the circuit using statistical models of the gates
 - Does not account for correlation between signal values
 - No accounting for glitching activity
- **Simulation based:**
Obtains toggle statistics from gate level simulations
 - Most accurate method
 - Slow

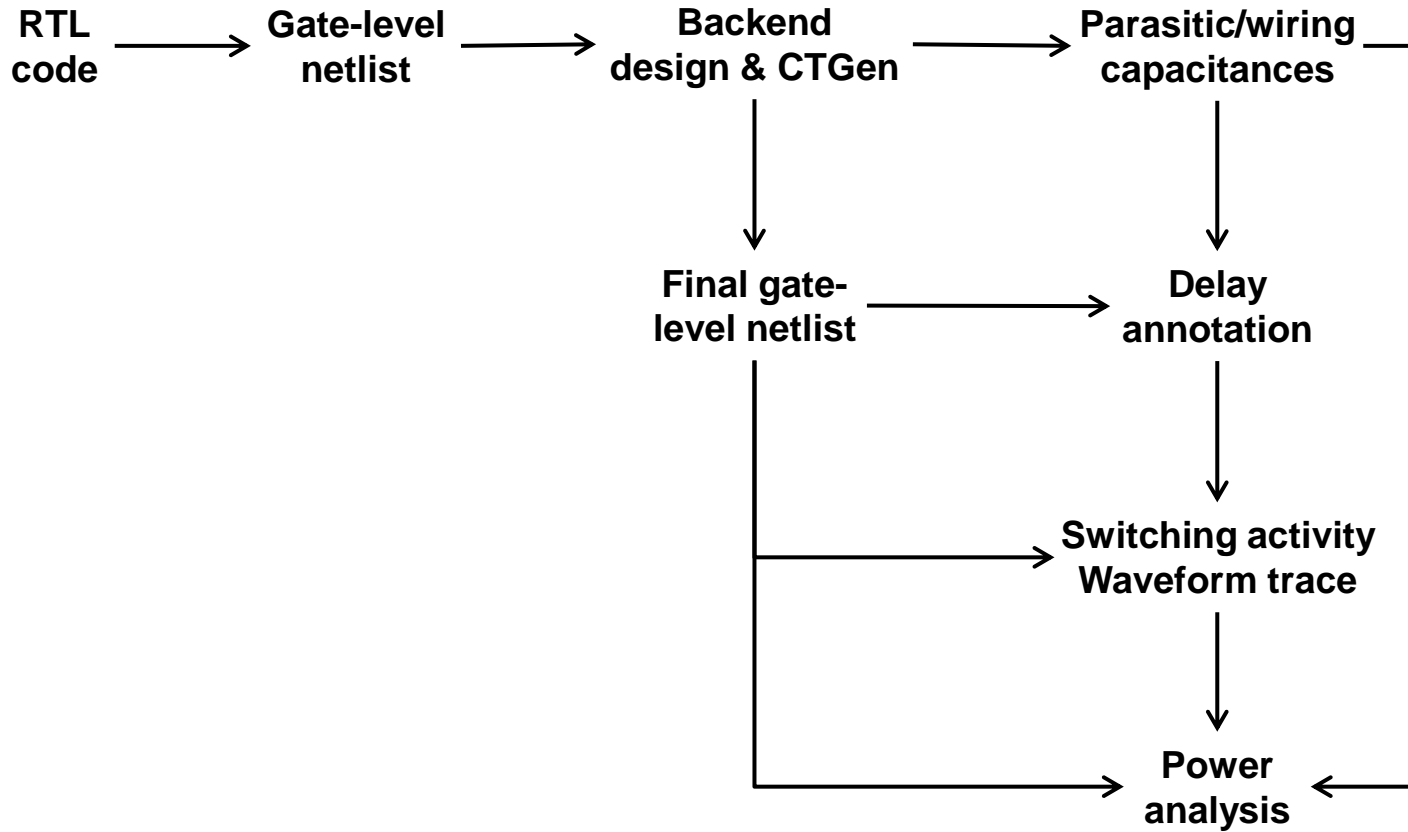


Leakage Power Consumption

   - Transistors leak currents even when in off-state
- Sources for leakage
 - Sub-threshold leakage
 - Dominant component in most circuits
 - Gate tunneling
 - Generally low, even in modern technologies due to high-k gate dielectrics
 - Decreases very rapidly with decreasing V_{dd}
 - Junction current
 - Generally low
 - Decreases very rapidly with decreasing V_{dd}



Leakage Power

 
- Long channel deices (>130nm): $I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$
 - I_{DS} mostly independent from Drain-Source Voltage
 - Leakage current depends strongly on $V_{GS} - V_{th}$
 - Decreasing threshold voltage increases leakage



- Impact of technology scaling on sub-threshold leakage (<130nm)

- Drain-Induced Barrier Lowering (DIBL): V_{DS} modulates threshold voltage
- I_{DS} becomes a function of V_{DS}

 - $I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}+\lambda_{DS}V_{DS}}{v_t n}}$





$$I_{leak} = I_0 e^{\frac{-V_{th}+\lambda_{DS}V_{DD}}{v_t n}}$$

← Voltage scaling reduces leakage

Drain current depends exponentially on thermal voltage $v_t = kT/q$

$$I_{DS} = I_0 e^{\frac{V_{GS} - V_{th}}{v_t n}} \quad n < 0$$

  - Exponential I_{DS} increase with temperature



Example: 0.7V, 100nm process, 15mm² die

- Stacking occurs



- In many logic gates (> 1 input)
- When introduced intentionally for leakage reduction

Leakage Reduction	
2 NMOS	9
3 NMOS	17
4 NMOS	24
2 PMOS	8
3 PMOS	12
4 PMOS	16


$$I_{leak,M1} = I_0 e^{\frac{-V_M - V_{th} + \lambda_{DS}(V_{dd} - V_M)}{v_{tn}}}$$

$$I_{leak,M2} = I_0 e^{\frac{-V_{th} + \lambda_{DS}V_M}{v_{tn}}}$$


Small speed penalty: ~25%

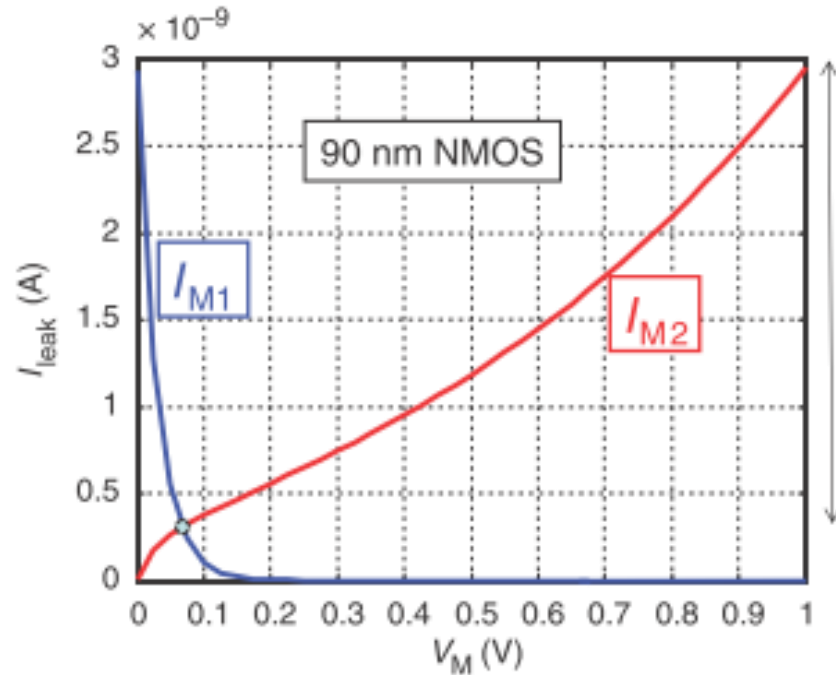 

 - Devices with different threshold voltages => can often be combined on same die/wafer
- Different process flavors (can typically not be mixed on same wafer)



M. Bohr, Intel Developer Forum 2009

 

Transistor Type	Logic (option for HP or SP)		Low Power	HV I/O (option for 1.8 or 3.3 V)	
	HP	SP	LP	1.8V	3.3V
EOT(nm)	0.95	0.95	0.95	~ 4	~ 7
Vdd (V)	.75/ 1	.75/ 1	0.75/1.2	1.5 /1.8	1.5 /3.3
Pitch(nm)	112.5	112.5	126	min. 338	min. 675
Lgate (nm)	30	34	46	>140	>320
NMOS Idsat (mA/um)	1.53 @ 1V	1.12 @ 1V	0.71 @ 1V	0.68 1.8 V	0.7 3.3 V
PMOS Idsat (mA/um)	1.23 @ 1V	0.87 @ 1V	0.55 @ 1V	0.59 1.8 V	.34 @3.3 V
Ioff (nA/um)	100	1	0.03	0.1	<0.01


- Sometimes IO transistors are an interesting option: low-leakage, high-VT but large distance to core transistors in the layout required

- Modern process technologies support devices with different threshold voltages
 - Typically three flavors: low-VT, standard-VT, high-VT
 - Often all three flavors can be mixed in the same design
- **VT-selection:** tradeoff between speed and leakage

$$t_{pd} = \frac{t_{OX}}{\mu\epsilon_{OX}} \frac{L}{W} C_L \frac{V_{DD}}{(V_{DD} - V_{th})^\alpha}$$


$$I_{leak} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_{DS}}{v_t n}}$$

- **Example:** 55nm process

 


Delay
Leakage

20ps
30nW

 

16ps
60nW

 


14ps
200nW

- Small increase in speed comes with a significant leakage penalty

- **Design tradeoff when choosing a VT flavor:**
 - Less leakage (high-VT) increases delay and vice versa
 - **Threshold voltage types can often be mixed**

- **Multi-VT design**

 

- Use low-VT cells only on critical paths
- High-VT cells are used in all other paths

Caveat: can be very problematic for near-VT or sub-VT design: path delays scale very differently

- **Methodology:**

- Either done by replacing non-critical cells in the backend OR already during synthesis by providing multiple libraries (HVT/SVT *and* LVT)



- Body of the transistor is often connected to the source (no body bias)

- Introducing a body bias modulates threshold voltage
 - Forward Body Bias (FBB): increases threshold voltage
 - Reverse Body Bias (RBB): reduces threshold voltage


- $V_{th} = V_{th0} - \lambda_{BS}V_{BS}$

- **BULK CMOS:**

 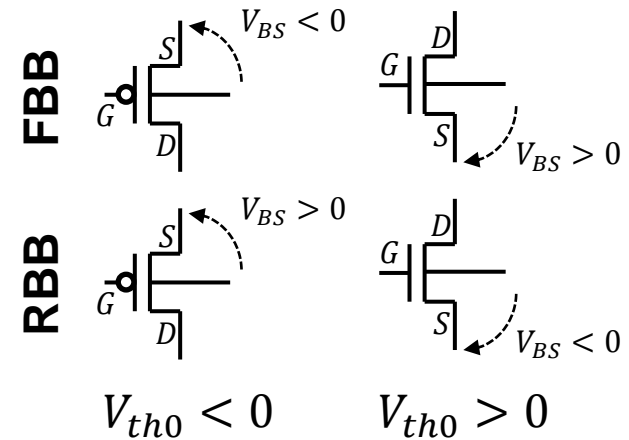- Effect of body bias decreases for technologies below 100nm
- FBB is limited to ~300mV to avoid operating junction diodes in forward direction






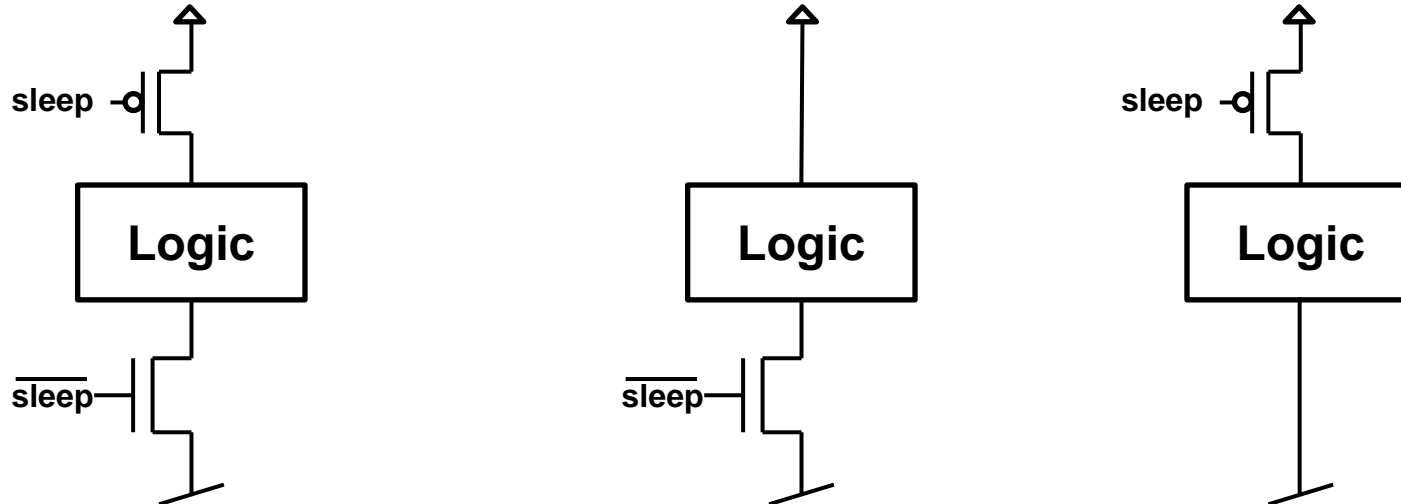- Avoid leakage almost completely when individual design units are not used:
 - Disconnect entire modules from the supply with headers and/or footers)



- Objectives with conflicting requirements
 - Sleep mode: large off-resistance to avoid leakage (stacking)
 - PMOS preferred over NMOS and HVT over LVT, header+footer
 - Active mode: minimize on-resistance to reduce negative impact on timing
 - Sleep transistors require large area
 - NMOS preferred over PMOS, LVT over HVT, footer-only

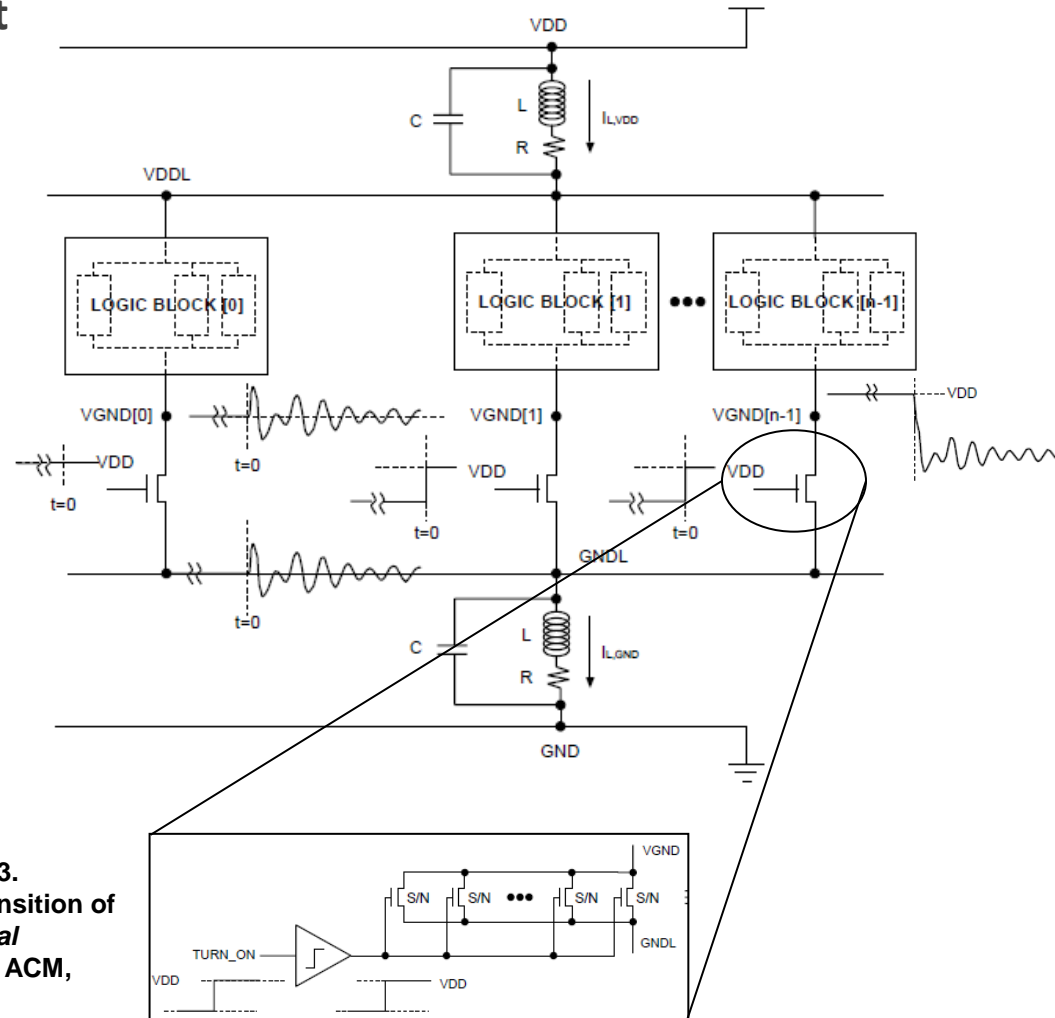  
- Rapid re-activation of a power gated block can cause large spikes on the supply network of the entire circuit
- Popular solutions:



Suhwan Kim, Stephen V. Kosonocky, and Daniel R. Knebel. 2003. Understanding and minimizing ground bounce during mode transition of power gating structures. In *Proceedings of the 2003 international symposium on Low power electronics and design (ISLPED '03)*. ACM, New York, NY, USA, 22-25. DOI=10.1145/871506.871515 <http://doi.acm.org/10.1145/871506.871515>


Voltage Scaling and Sub-VT Design
 
$$E = \int \frac{C_L V_{dd}^2}{2} \beta f_{clk} + V_{dd} I_{leak} dt$$



Minimize leakage energy by:

 
- **Reducing voltage**
- Reducing V_{dd} to GND paths



Minimize active energy by:

- **Reducing voltage**
- Switching activity
- Capacitance
 
$$E = \int \frac{C_L V_{dd}^2}{2} \beta f_{clk} + V_{dd} I_{leak} dt$$



- Reducing supply voltage below nominal
 - Most popular and most effective low-power strategy
 - Voltage-scaling
 - Reduces active power
 - Reduces leakage power (but not necessarily energy/Op)
 - Reduces speed : need to compensate with architectural changes (e.g., parallel processing)

- Inverter Delay

$$t_{pHL} = 0.69 \frac{3 V_{DD} C_{load}}{4 I_{DSATn}} = 0.52 \frac{V_{DD} C_{load}}{k_n V_{DSATn} \left(V_{DD} - V_{THn} - V_{DSATn}/2 \right)}$$


- Delay is a function of the supply voltage above V_{Th}


- *Depends strongly on the overdrive*
- *Decreases as overdrive decreases*

- Delay in the sub- V_{Th} regime

- *Exponential dependency on overdrive*
 
$$t_{pd} \propto \frac{V_{DD} C_{load}}{I_0 e^{\frac{V_{DD} - V_{th}}{v_{tn}}}}$$



 


Energy per operation as a function of voltage and clock rate

Observation: better energy efficiency for higher frequency at constant voltage.


- Reduced overhead per operation due to constant (leakage) currents

- Near/below V_T operation:
 - Exponential delay/leakage increase
 - Minimum energy voltage: balance between leakage and active power consumption

J. Rodrigues, PATMOS 2011, Keynote

 

Relatively flat around EMV

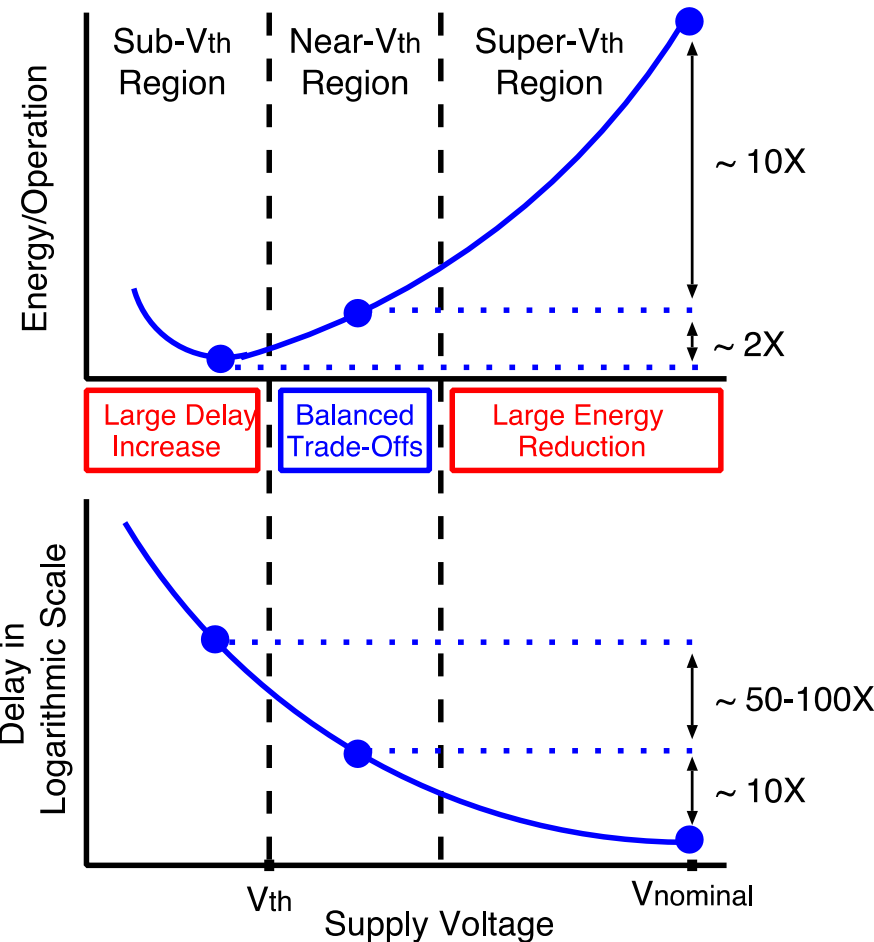

- Real-time embedded system requirements
 - Handle a given workload with lowest power consumption
- Optimum solution
 - Operation at the energy minimum voltage with power gating during idle periods to avoid leakage
 - But, power gating is only effective when idle periods are long and memories can often not be power gated and are the major source of leakage


Operation @ EMV



with power gating



without power gating

 


**Operation below EMV
without power gating**





Example:

**Power Consumption and Energy
Efficiency in Memories**

Active power

 

Leakage power

  

typical embedded processor

- For embedded processors, memories occupy a large percentage of the silicon area
- Active mode:
 - Data and program memory can consume 2/3 of total power
 - Low-frequency: SRAM leakage becomes visible
- Sleep modes:
 - Generally, no power gating to retain SRAM content
 - SRAM leakage becomes dominates system power consumption (3-4 pJ/bit in 180nm):
32kByte -> 400nW @ 1.8V

Example: Standard Cell Based Low Power Memory



Write Logic


- *Clock-gates (b)*: smaller and less power than *enable flip-flops (a)*

Read Logic

- Above-VT
 - ✓ *Multiplexers (c)*: smaller, faster, and less power than tri-state buffers
- Sub-VT
 - ✓ *Tri-state buffers (d)*: less leakage (energy) than multiplexers


Array of Storage Cells

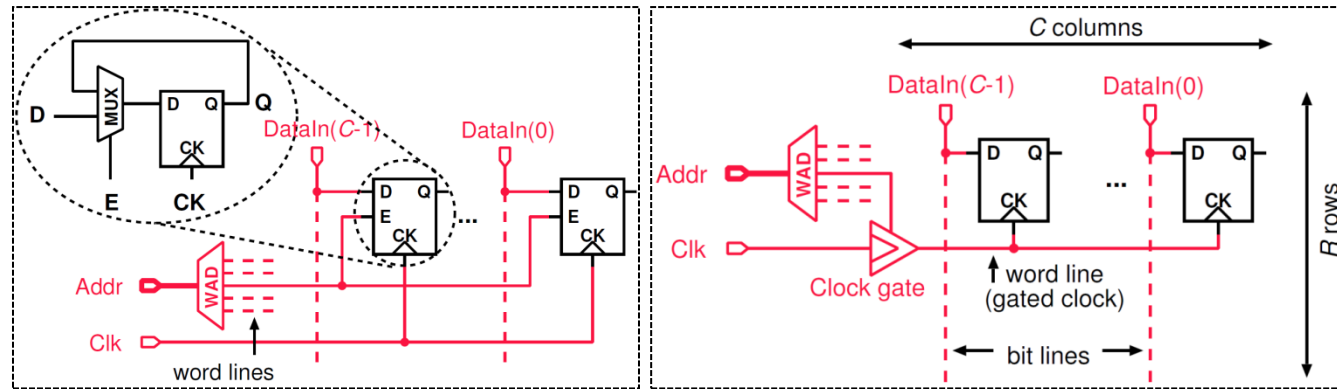- *Latch arrays* smaller than *flip-flop arrays*, but longer write-address setup time



(a) Enable flip-flops

(b) Clock

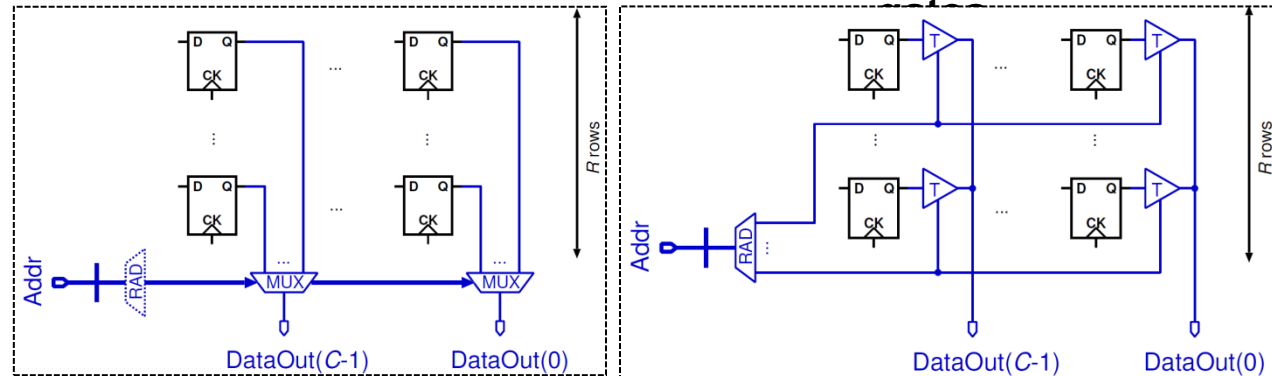



(c) Multiplexers

(d) Tri-state buffers

Large memory arrays: little switching activity

- **Total energy is dominated by leakage**
- **Active energy negligible, except for smallest SCMs**
- **Only smallest SCMs reach EMV in sub- V_T domain**

➔ **Minimize leakage!**

 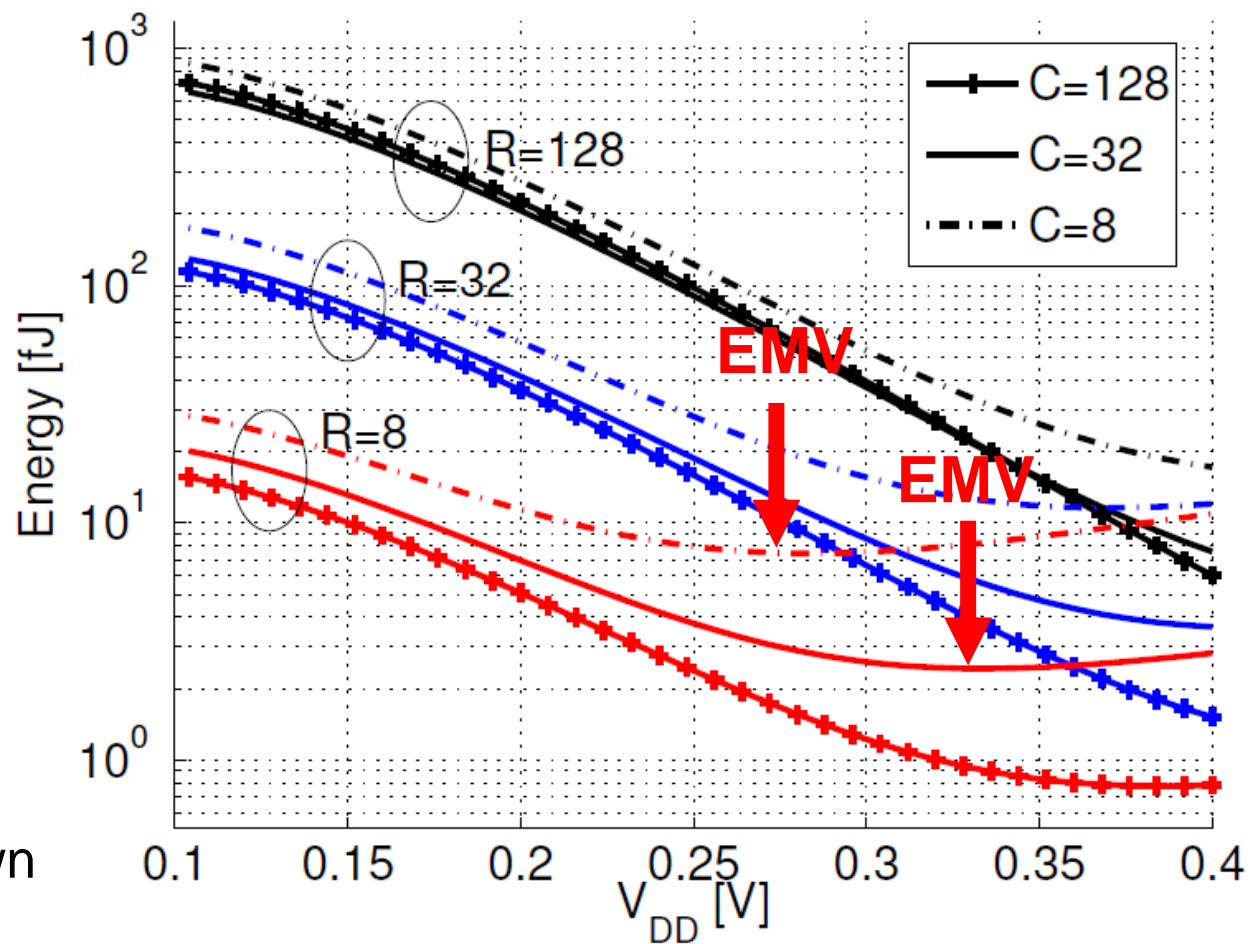

P. Meinerzhagen *et al.*, JETCAS'11


Chip microphotograph and zoomed-in layout picture

Area cost of $12.7 \mu\text{m}^2$ per bit (including peripherals)

Scan-chain test interface


Functionality verification:
W/R random and checker-board patterns

Oven to control temperature:
 27 or 37°C

 

Measured energy per bit-access performed at maximum speed

 Measured energy minimum is 14fJ/bit at 500mV, 110kHz



At $V_{DDhold}=220mV$, data is correctly held with a leakage power of 425-500fW per bit (best and worst out of 4 measured dies)

At 37°C (typical for biomedical implants)

- $V_{DDmin}=400mV$ (instead of 420mV at 27°C)
- Maximum operating frequency doubles
- But: higher leakage power
- Low retention voltage is key for low power

